

Name: Li Xianzhe

Student ID number: 2022214880

Score: _____ / 100

Laboratory #5 – Thevenin Equivalent Circuits & Maximum Power Transfer

EE188L Electrical Engineering I
NAU & CQUPT – Fall 2021

Objectives

1. Use voltage measurements and calculations to determine the Thevenin equivalent for a given circuit in the laboratory
2. Investigate the relationships between source resistance and load resistance for maximum power transfer.

Grading:

Activity #1 _____ / 20



Activity #2 _____ / 20

Material

1. DC Power source, breadboard, DMM, jumpers
2. Resistors: $6.8k\Omega$ (2), $1.8k\Omega$, 22k, 10k, 1k, 470 ohms. Also, the calculated resistor R_{TH}

Important Concepts

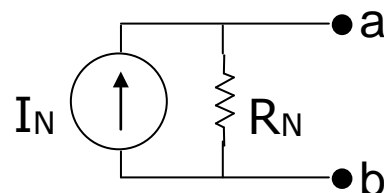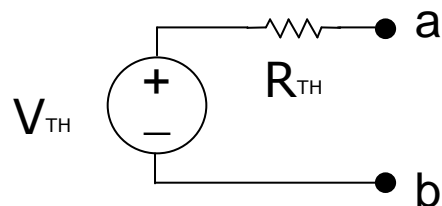
1. **Thevenin Equivalent Circuit** – Any linear circuit connected to two terminals can be replaced by an equivalent circuit consisting of a voltage source (V_{TH}) in series with a resistor (R_{TH}) that connect to the two terminals in place of the original circuit. All voltages and currents that can be measured at the two terminals are the same for the original circuit and for the replacement equivalent circuit.



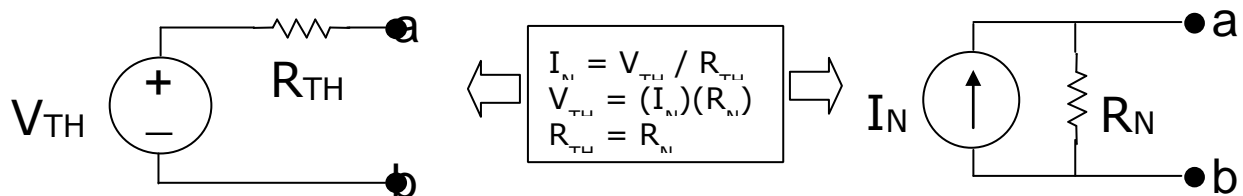2. **Norton Equivalent Circuit** – Any linear circuit connected to two terminals can be replaced by an equivalent circuit consisting of a current source in parallel with a resistor.
3. **Maximum Power Transfer** – When a linear circuit with a given R_{TH} or R_N is delivering power to a load resistor, the power delivered to the load is maximum when the load resistance equals the Thevenin equivalent resistance (R_{TH}) or the Norton equivalent resistance (R_N) of the linear circuit.

Background

Source Transformation – A Thevenin Equivalent circuit can be replaced by a Norton Equivalent circuit and vice versa.



Thevenin Equivalent Voltage (V_{TH}) – In all cases this voltage is equal to the voltage at the circuit terminals with no external load connected. This is sometimes called the “open-circuit” voltage.

Norton Equivalent Current (I_N) – In all cases this current is equal to the current that would flow through a wire connected between the circuit terminals. This is sometimes called the “short-circuit” current. This method must not be used to test an actual circuit if the short would burn out the circuit or cause it to operate outside its linear range.

Thevenin or Norton Equivalent Resistance (R_{TH} or R_N) – The methods for determining R_{TH} or R_N depend on the type of voltage and current sources contained in the circuit:

1. Circuits with **Independent Sources ONLY** (no dependent sources) – There are three methods:
 - a) By Source Removal – First set all sources to a zero value; this is equivalent to replacing all voltage sources with a wire (a “short”) and removing all current sources (leaving an “open” circuit). Second, determine the equivalent resistance of the remaining circuit by “looking into” the terminals; the equivalent resistance is the value of R_{TH} or R_N .
 - b) By Short-Circuit Current – This method applies during analysis of a circuit or in testing an actual circuit that can safely have a short circuit at its terminals. First, determine the voltage at the terminals with no load connected; this is

V_{TH} . Second, determine what current would flow through a wire connected between the terminals; this is the short-circuit current (I_{sc}). R_{TH} can then be calculated:

$$R_{TH} = V_{TH} / I_{sc}$$



$$R_N = R_{TH}$$

- c) By Applying a Load – This method applies when testing an actual circuit to find its equivalent source resistance (R_{TH} or R_N). First, measure the voltage at the terminals with no load connected; this is V_{TH} . Second, connect a load resistor to the circuit terminals; the load resistor (R_L) should be low enough to cause a measurable voltage drop from no-load conditions, but not so low as to cause the circuit to malfunction or operate outside of its linear range. R_{TH} can then be calculated:

$$R_{TH} = (V_{TH} - V_L) \cdot (R_L) / (V_L) \quad R_N = R_{TH}$$

Maximum Power Transfer

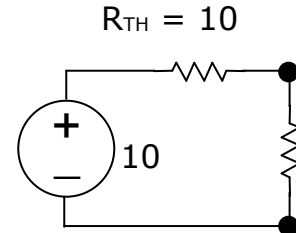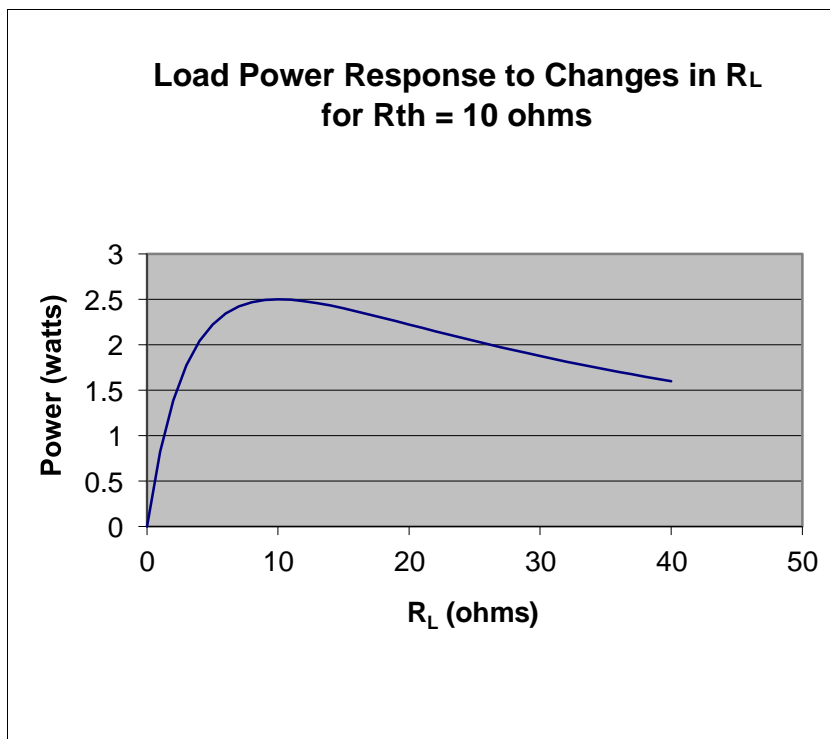Given an existing circuit with a Thevenin resistance (R_{TH}), the maximum power is transferred to the load resistor (R_L) when the value of the load resistor is selected to match the value of the Thevenin resistance (R_{TH}) of the power source. Figure 1 demonstrates this for a value of $R_{TH} = 10 \Omega$.



$$P = I^2 \cdot R$$

$$= V^2 / R$$


Figure 1

Activity #1 – Thevenin Equivalent of the given circuit

In this activity, you will determine the Thevenin equivalent circuit values (V_{TH} and R_{TH}) for the circuit below on your lab bench by performing measurements and some calculations using method 1a and 1b, as explained earlier.


1. Get the 3 resistors shown in the circuit and connect them on the breadboard as shown in the circuit diagram below.
2. **Do NOT yet connect the dc power supply!** Place a short-circuit (wire) across what will be the source voltage terminals, and **measure the R_{in}** with your DMM, looking into the circuit from the load side. **This measured resistance is R_{TH}** Remove the short after the resistance measurement!

$R_{TH} =$ 5.165k Ω

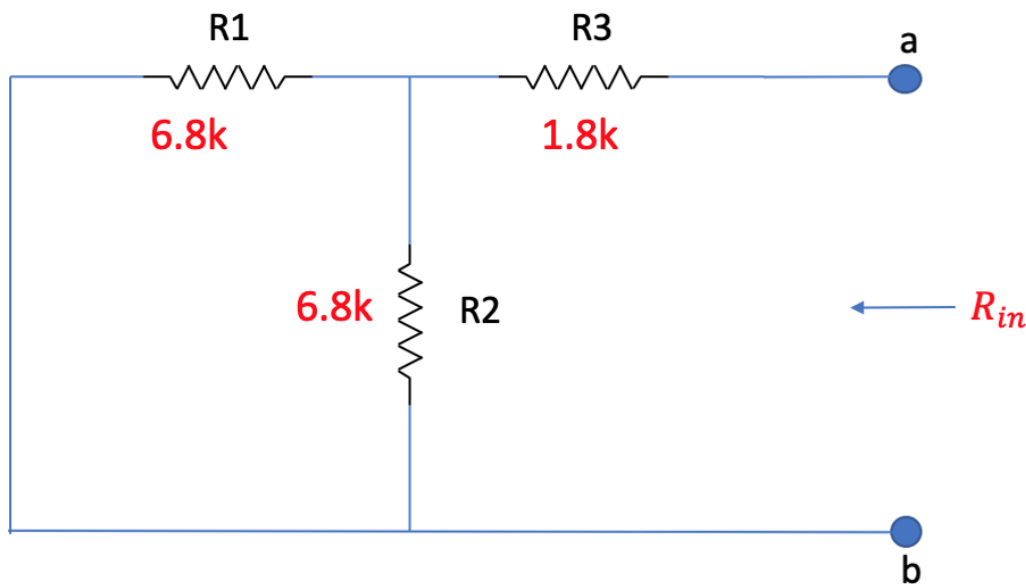

3. Now, adjust the dc power source to read 20 volts on one of the output channels and connect it to the circuit, as shown below. There should be no load resistor connected to the output (terminals a & b) yet.
4. Accurately measure and record the (open-circuit, **without** R_L connected) output voltage V_{oc} at terminals a & b.

V_{oc} with no load = $V_{TH} =$ 10.085V

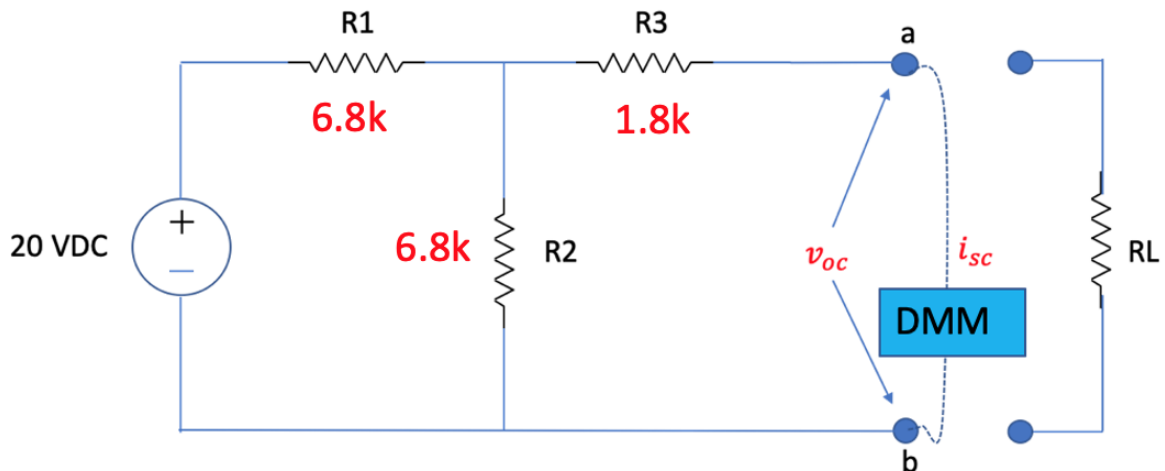


5. Next, **still without RL connected**, measure the short-circuit current (I_{sc}) between terminals a & b. To do this, set the DMM to measure Milliamps and connect it across terminals a & b. **This ensures that the DMM is in series within the short-circuit.**


Again, $R_{TH} = V_{TH} / I_{sc}$. Check that this value is the same as from Step 2 above.

$$R_{TH} = \frac{V_{TH}}{I_{sc}} = \frac{10.085}{(1.977 \times 10^{-3})} = 5.101 K\Omega$$

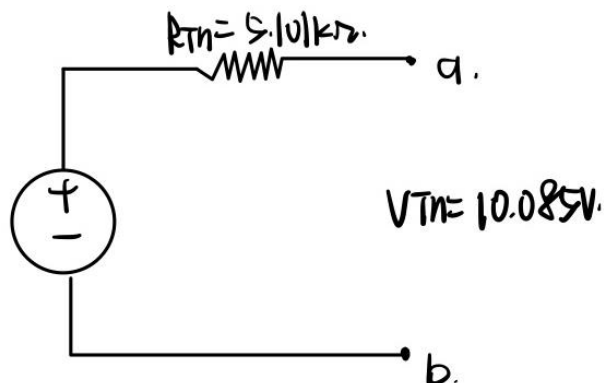6. Draw the Thevenin equivalent circuit for the function generator output showing values for V_{TH} and R_{TH} based on your measurements and calculations.



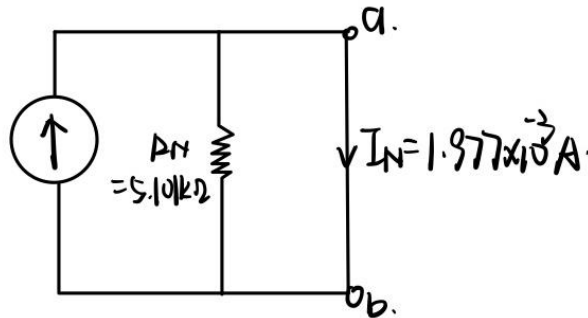7. Using your values for V_{TH} and R_{TH} , calculate the Norton equivalent circuit values I_N and R_N . Draw the Norton equivalent circuit for the function generator output showing values for I_N and R_N .



Activity #2 – Maximum Power Transfer

1. With the same circuit setup used in Activity #1, now connect the load resistance between terminals a & b. Measure and record the output voltage (at terminals a & b) with **Use different load resistors to act as the load (R_L)**. The resistance values to use are as shown in the table below.

One of the resistors to use should equal the R_{TH} in value!

Load Resistance (Ω)	Output Voltage (V_L)	Calculated Power to the Load (watts)
470 ohms	0.825V	$1.44 \times 10^{-3} W$
1.0k	1.619V	$2.62 \times 10^{-3} W$
R_{TH}	4.992V	$4.88 \times 10^{-3} W$
10k	6.604V	$4.36 \times 10^{-3} W$
22k	8.123V	$3.00 \times 10^{-3} W$

2. Calculate the power delivered to the load for each of the test conditions and enter it in Table 1. (The equation for P_L is V^2/R .)
3. Plot the various values of power in the table, similar to Figure 1. Discuss how your measurement results compare with the concept of Maximum Power Transfer:

Discussion:

When $R_L = R_{TH}$, the power is greater than other R_L values, and the measurement results are basically consistent with the concept of maximum power delivery. In other words, when the resistance of the load is equal to the equivalent resistance of the original circuit, the power is maximized.


Have your lab instructor or lab aide sign below after they have checked your progress.

Signature _____ Date _____

Again, $R_{TH} = V_{TH} / I_{sc}$. Check that this value is the same as from Step 2 above.

$R_{TH} = 5.101 \text{ k}\Omega$

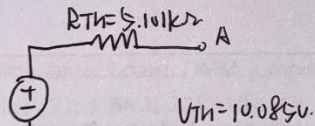6. Draw the Thevenin equivalent circuit for the function generator output showing values for V_{TH} and R_{TH} based on your measurements and calculations.



Name: Li Xianzhe Student ID number: 202214880

Score: _____ / 100

Laboratory #5 –
Thevenin Equivalent Circuits &
Maximum Power Transfer
EE188L Electrical Engineering I
NAU & CQPT – Fall 2023

30/10