

Lab Section (Day/Time) 10.13/14:00

Names of Student with ID#

Student Li Xianzhe 2022214880

Marks _____

EE 188L - Lab 6

Introduction to Operational Amplifier Circuits

NAU + CQUPT (Fall 2020)

I. Introduction

The **Operational Amplifier (Op-Amp)** is a highly-sophisticated (complicated) **solid-state** (Transistors → next semester in EE 280) circuit **designed** to be used in many applications to make **mathematical relationships** between **input electrical signals** and **output electrical signals**. It is used primarily in **instrumentation** that produces **output voltage signals** that are a **mathematical function** of the **input voltage signals** [$V_{\text{out}} = f(V_{\text{in}})$].

The **basic properties** of the **ideal op-amp** have been introduced and discussed in class, along with **additional details and results** of those basic properties. Some of the **results** are not obvious at the first time that the student has seen them.

The **op-amp** has **2 DC voltage inputs** that supply **DC voltages** to it which **power** the transistor circuits inside—sometimes these are not shown in schematics. The **op-amp** has **2 signal inputs** and **1 signal output**. Additional ports (connections from inside the **op-amp** circuit to outside) may exist for some **op-amps**, but this lab does not require those.

As explained in class the **ports** and **properties** of the **ideal op-amp** are:


- $v_p \Rightarrow$ **noninverting input** with respect to ground.
- $v_n \Rightarrow$ **inverting input** with respect to ground.

- $v_d = v_p - v_n \Rightarrow$ **difference input voltage** (Note: **not** with respect to ground).
- $v_o \Rightarrow$ **output** with respect to ground.
- $R_{in} = \infty \Rightarrow$ **input resistance between v_p and v_n** ; this results that the **currents into the input ports i^+ & $i^- = 0$** .
- $R_{out} = 0 \Rightarrow$ **output resistance at the v_o port**
The R_{in} & R_{out} values \rightarrow **no loading at the inputs or output.**
- $A_{vo} = \infty$ **with infinite bandwidth (BW)**
- **No offset output voltage** \rightarrow if v_d , v_p & v_n **all = 0**, then $v_o = 0$
- And an **external negative feedback path**.

The last “**property**” of the **ideal op-amp** is actually a fundamental of its design, which is its **external negative feedback (NFB) circuit path** from the **output port** to its **inverting input port** (the “**secret of the op-amp**”):

The **op-amp senses** the **voltages** at v_p and at $v_n \rightarrow$ If $v_d = v_p - v_n$ ever starts to become **not = to 0**, the op-amp provides *whatever it can*, through the **feedback path**, to **drive $v_d = v_p - v_n$ back to zero!**

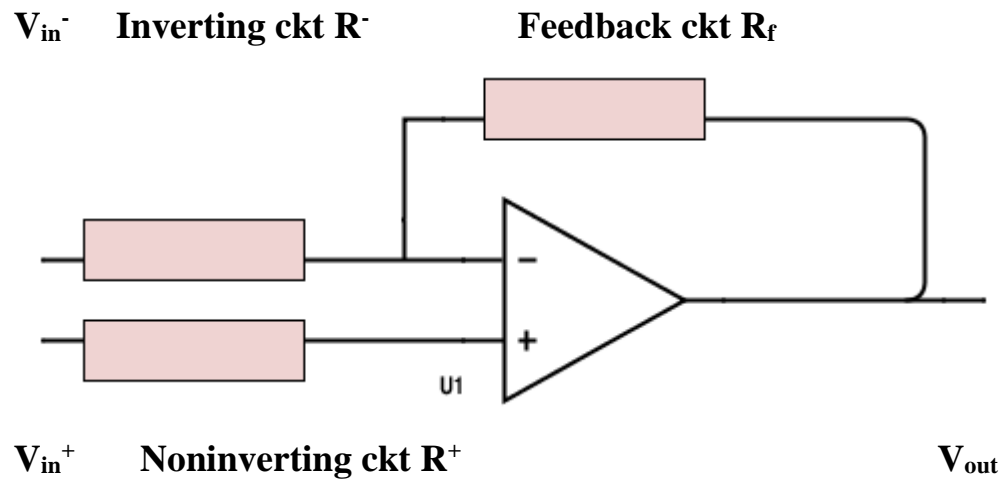A **block diagram** of a **general op-amp feedback system** is shown below. An **input circuit R^-** goes to the **inverting input**; an **input circuit R^+** goes to the **noninverting input**; and a **feedback circuit Z_f** goes between the **output** and the **inverting input**, providing the **NFB path**.



A brief **Table** of these properties of a **real Op-Amp** is given below. **Slew rate** and **CMRR** are additional properties that are not covered at this time. **100 dB = 10^5**

Parameter	Symbol	Ideal Op-Amp	Practical Op-Amp
DC Open loop gain	A_{OL}	∞	100 dB
Input Impedance	Z_{IN}	∞	2M Ω
Output Impedance	Z_{out}	0	75 Ω
Input Offset Voltage	V_{IO}	0	1mV
Slew rate	SR	∞	Depends on input signal frequency
Bandwidth	BW	∞	Depends on input signal frequency
CMRR	ρ	∞	90 dB

II. Circuits and equipment


OBJECTIVE:

To become familiar with the use and characteristics of a **741 op-amp** as an **ideal op-amp**, by building and testing the following circuits:

- Inverting Amplifier
- Non-inverting Amplifier
- Summing Inverting Amplifier
- Difference Amplifier

MATERIALS:

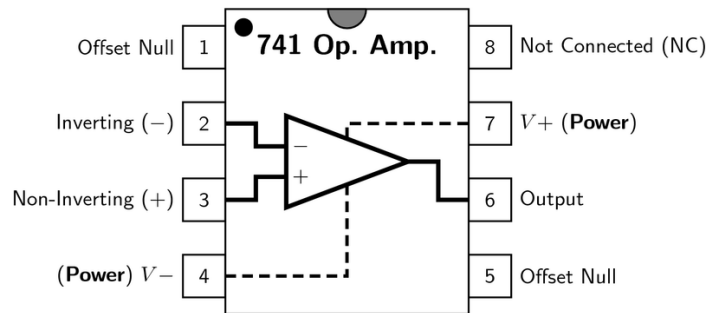1. **741 Op-Amp**
2. Assorted Resistors
3. Function Generator
4. Digital Multimeter
5. Dual Channel Oscilloscope
6. Multiple output DC Power Supply




PROCEDURE:

Comments:

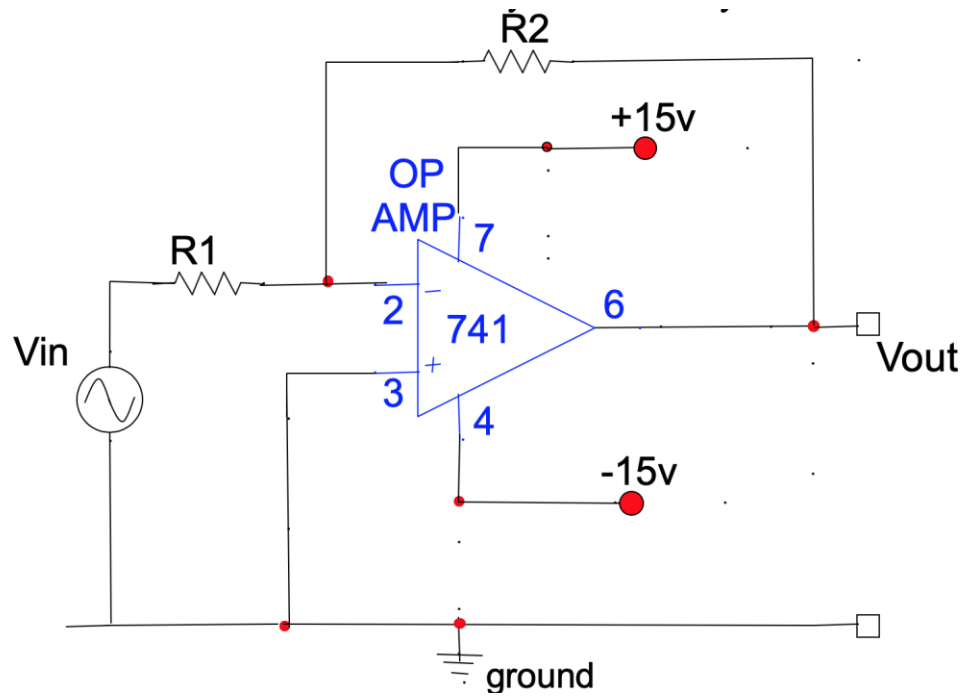- 1) Use +/- 15 volts for the Op-Amp DC voltages on pins 7 & 4. Follow the instructions on creating +/- voltages!!
- 2) Use 0.01 to 1.0 AC sine wave signals, depending on the circuit amplifier gains.
- 3) The first 3 circuits use the same values for R_{in} and R_f : thus you will not need to completely rebuild each circuit from the beginning. The last one has given values for the resistors.
- 4) The labels for resistors may be different on the figures. You can figure out which is R_f and which is R_{in} , etc.

Sample circuit for an **inverting amplifier**:




Circuits to be built today:

A. Inverting Amplifier

- **Design** a combination of R_F and R_{in} (Note: not the same R_{in} as the input impedance of the ideal op-amp) for a calculated gain of **-10**; and record the calculated **gain** V_o/V_i , for the circuit shown below. Assume an ideal op-amp. Use $k\Omega$ ranges.

$R_F = 10\text{ k}\Omega$ and $R_{in} = 1\text{ k}\Omega$

- Construct the circuit shown below, referring to the **figure above** for the **pin-out configuration** of the **741 op-amp**.
- For $f = 100\text{Hz}$, use a **sine wave** from the **FG**. Adjust the input to **$0.4V_{p-p}$** (peak-to-peak).
 - a) Measure and record **voltage gain** V_o/V_{in} . Compare with calculated value. Use **peak values**. **Measured gain = -10.2**.
 - b) Find the **maximum peak-to-peak output voltage** without **distortion** by increasing the input voltage until V_o begins to clip: it should be a bit below the **$\pm 15V_{DC}$ power sources** at pins **4 & 7**.
 - c) **Max input $V_{pp} = 2.96V$** . **Max output $V_{pp} = 27.6V$** .

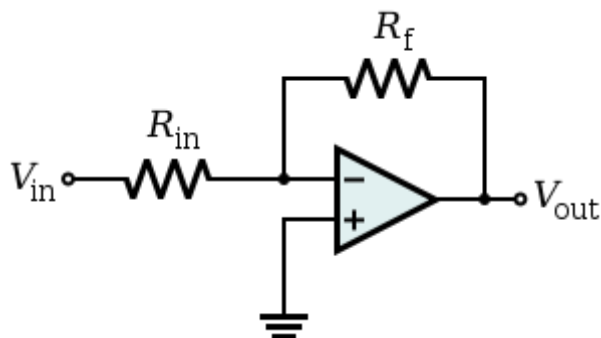


$R_{in} = 0.99\text{ k}\Omega$ $R_f = 10.1\text{ k}\Omega$

- How were you able to find that the output is ‘inverted’?

Explain: By looking at the phase of the input and output waveforms in the oscilloscope, a phase difference of 90° can be observed

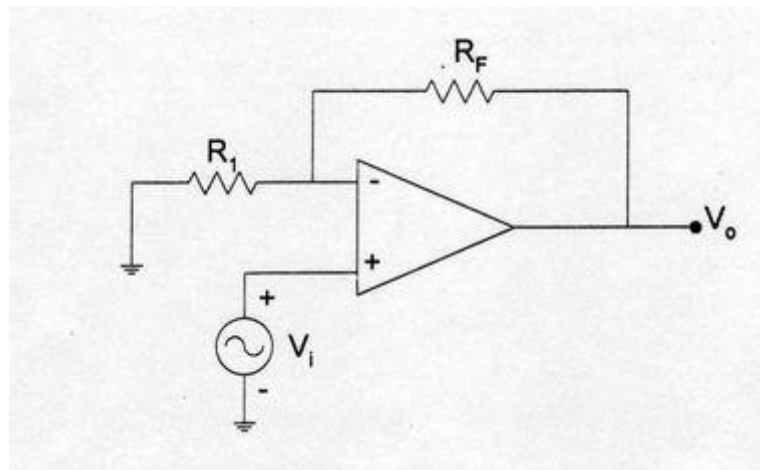B. Noninverting Amplifier

- **Design** a combination of R_F and R_1 for a calculated gain of **+11**; and record the calculated **gain** V_o/V_i for the circuit shown below. Assume an ideal op-amp. Use $k\Omega$ ranges.
 $R_1 = 1\ k\Omega$ and $R_F = 10\ k\Omega$
- Construct the circuit shown below, referring to the **figure above** for the **pin-out configuration** of the **741 op-amp**.
- For **$f = 100\text{Hz}$** , use a **sine wave** from the **FG**. Adjust the input to **$0.4V_{p-p}$** (peak-to-peak)
- Measure and record **voltage gain** V_o/V_{in} . Compare with calculated value. **Measured gain = 11.1**
- Find the **maximum peak-to-peak output voltage** without **distortion** by increasing the input voltage until V_o begins to clip: they should be a bit below the **$\pm 15V_{DC}$ power sources** at pins **4 & 7**.
Max output $V_{pp} = 28.0\text{ V}$. Max input $V_{pp} = 2.72\text{ V}$.



$R_1 = 10.1\ k\Omega$ $R_f = 0.99\ k\Omega$

- How were you able to find that the output is 'non-inverted'?
Explain: By looking at the phases of the input and output waveforms in the oscilloscope, it can be observed that their phases are the same and there is no phase difference

C. Difference Amplifier


- Design the difference amplifier below, which has a difference gain = 10.

Use k Ω range resistors. $R1=R3=1\text{ k}\Omega$, $R2=R4=10\text{ k}\Omega$

- Build it and verify the calculated difference gain
Measured gain= 10 .
- Using two channels of the FG, to produce two way input: For $f = 100\text{Hz}$, use a sine wave from the FG. Adjust the input to

$$V_{1pp} = 0.1\text{ V and } V_{2pp} = 0.5\text{ V}$$

- Output voltage $V_{pp} = 4.0\text{V}$

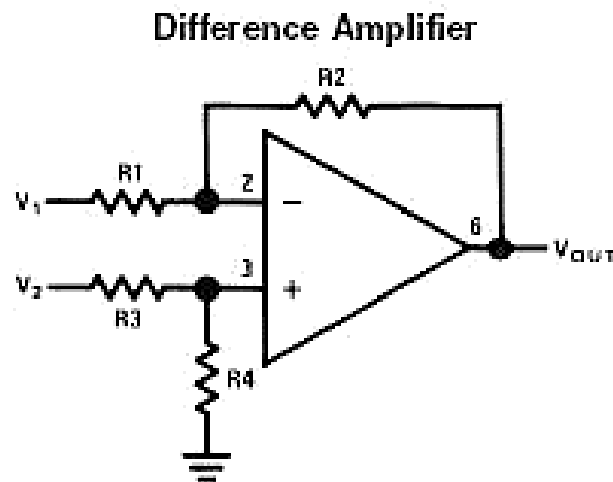

$$V_{OUT} = \left(\frac{R1 + R2}{R3 + R4} \right) \frac{R4}{R1} V_2 - \frac{R2}{R1} V_1$$

For $R1 = R3$ and $R2 = R4$

$$V_{OUT} = \frac{R2}{R1} (V_2 - V_1)$$

$$R1/R2 = R3/R4$$


$$R1=R3=10.1\text{ k}\Omega \quad R2=R4=0.99\text{ k}\Omega$$

- How were you able to find that the output is a 'difference'?

Explain: It can be observed that the output VPP is 10 times greater than the difference between the two inputs in the oscilloscope.

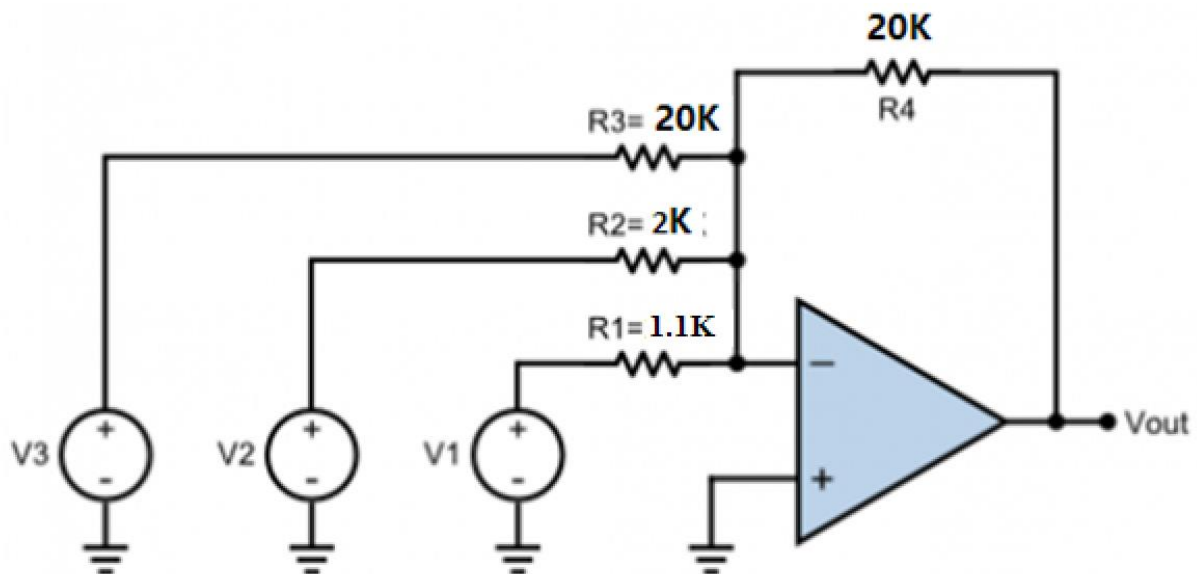D. Summing Amplifier

- Analyze the summing circuit below and determine the theoretical V_{out} as a function of the inputs V_1 , V_2 and V_3 .
theoretical $V_{out} = 583.6mV$
- Build it and verify by measurement the predicted output for $V_1 = V_2 = V_3 = 0.01$ Volts AC (Prof Du has changed the voltage requirement for these experiments to 0.02V), sine wave, $f=100Hz$.
→ Just apply the same voltage to all 3 inputs.
- Record output voltage $V_{pp} = 568mV$



- How were you able to find that the output is ‘summed’?

Explain: As can be seen, the output VPP is the weighted sum of the three inputs in the oscilloscope with R_4 .

Attachments:

Prof Du's signature:

Lab Section (Day/Time) _____

Names of Student with ID# Li Xianzhe

Student 202214880 Marks 13/10

EE 188L - Lab 6

Introduction to Operational Amplifier Circuits


NAU + CQUPT (Fall 2020)

Results of each experiment oscilloscope(as required by Prof Du)


A:




And its input is distort when maximum:

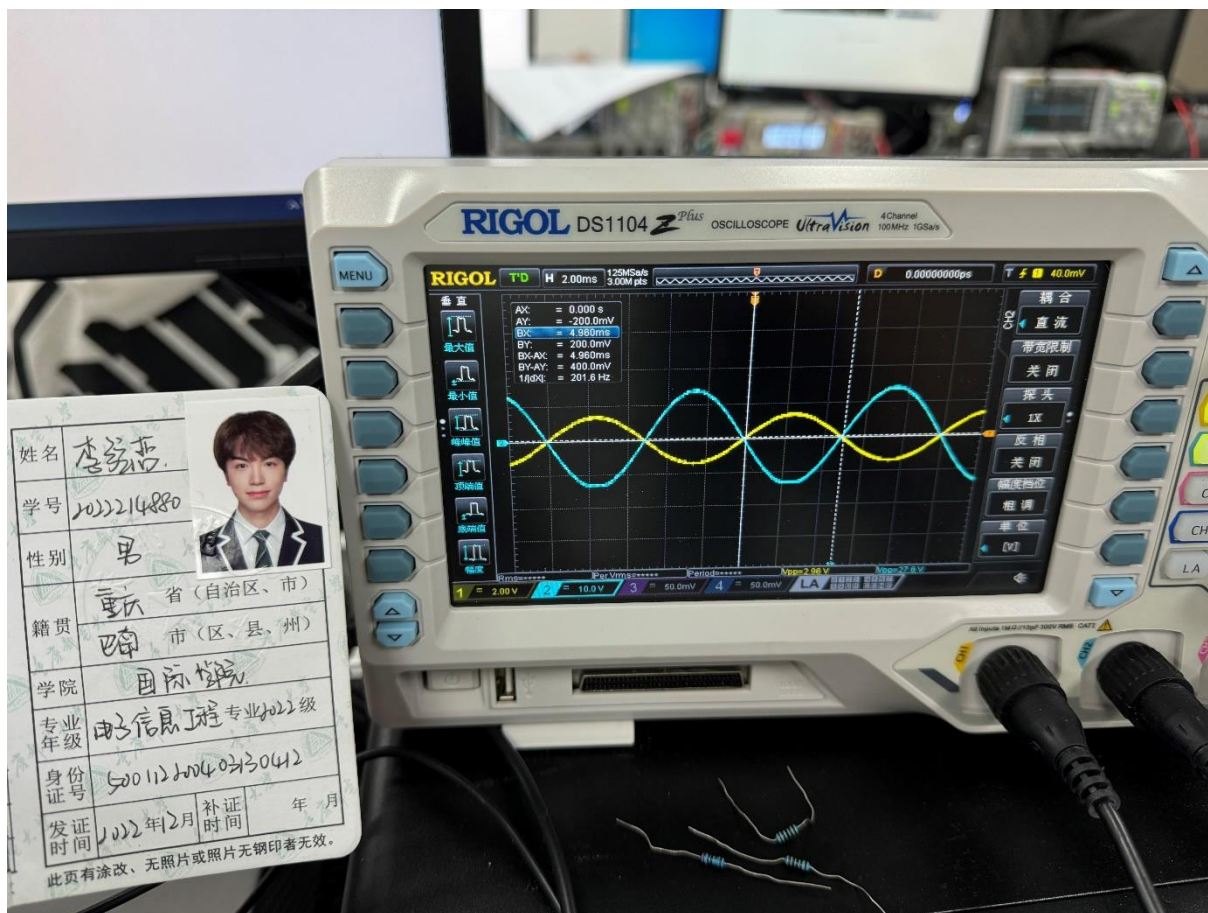


B:

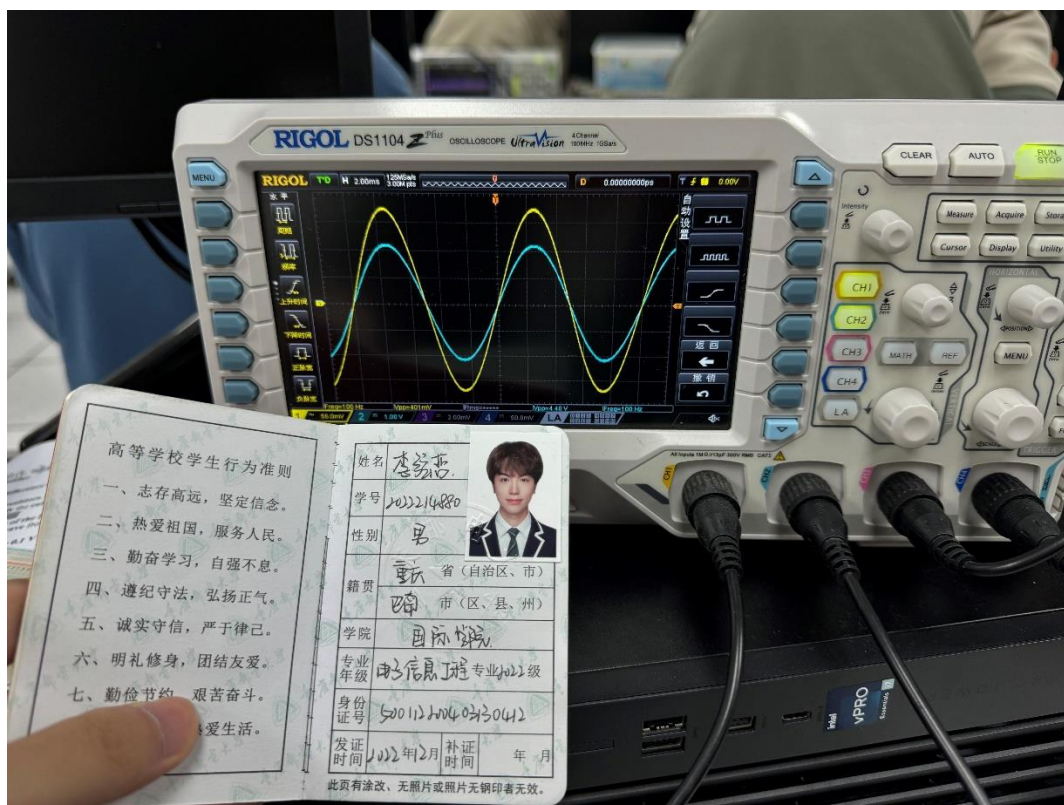

And its input is distort when maximum:

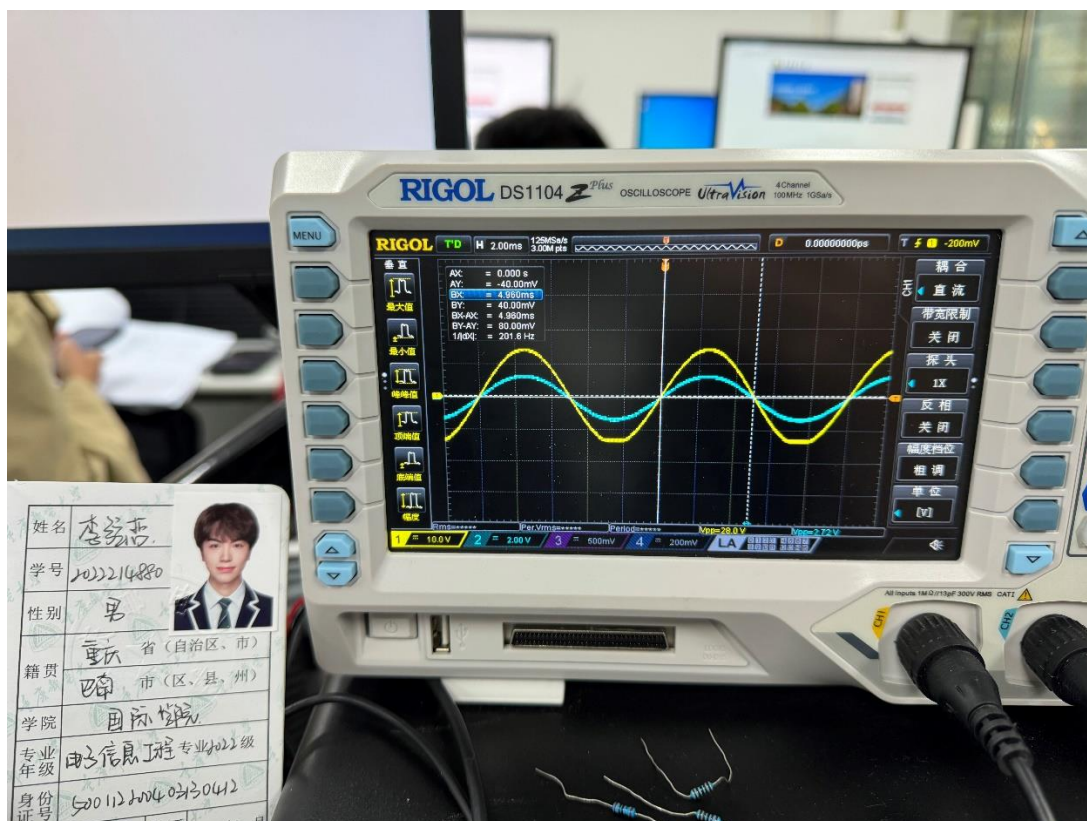

C:

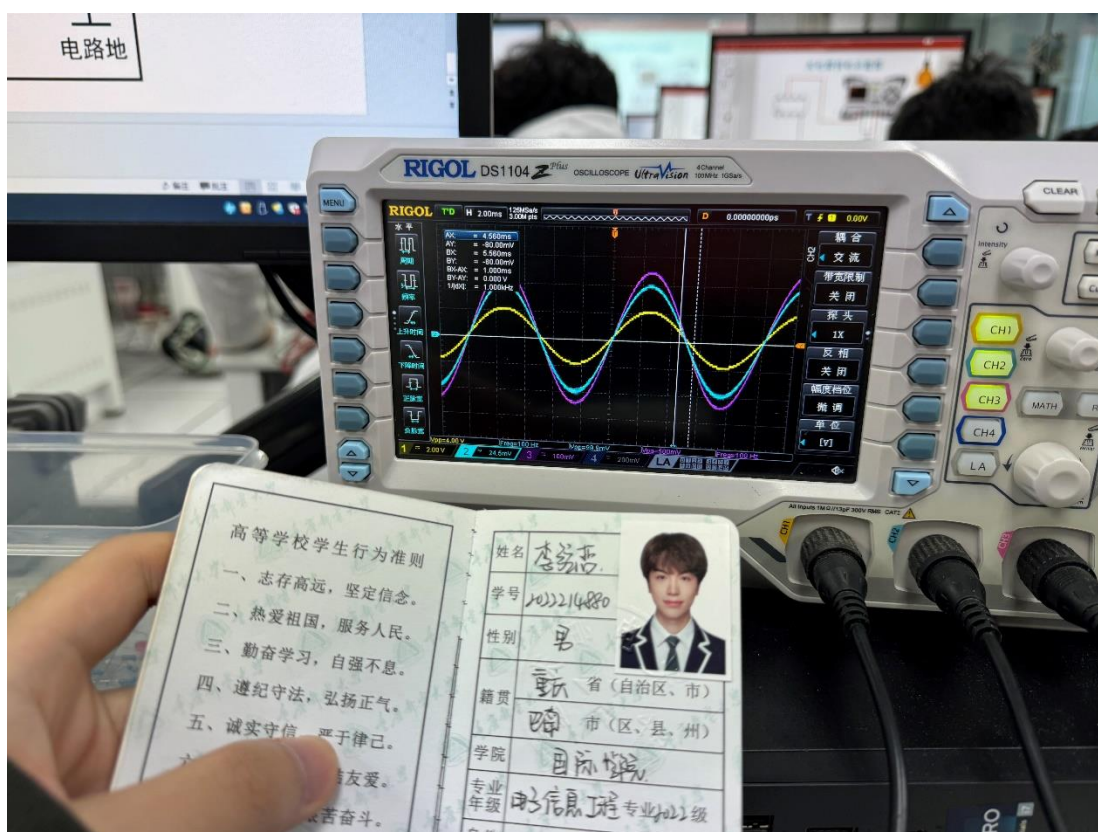

D:

