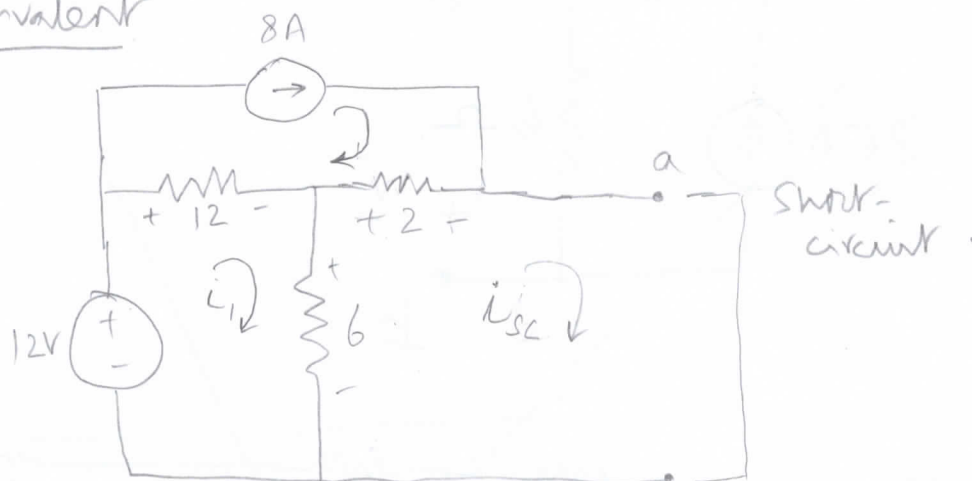


Pr 4.66

Chapter 4(B) Problems.

①

Find Norton Equivalent



We know $I_N = I_{sc}$

and $R_N = R_{in}$ with all sources set to zero.

to find I_{sc} :

writing mesh equations:

$$i_{12\Omega} = i_1 - 8$$

$$i_{6\Omega} = i_1 - i_{sc}$$

$$i_{2\Omega} = i_{sc} - 8$$

$$-12 + 12(i_1 - 8) + 6(i_1 - i_{sc}) = 0$$

$$-6(i_1 - i_{sc}) + 2(i_{sc} - 8) = 0 \quad (a) \quad 18i_1 - 6i_{sc} = +108 \rightarrow ①$$

$$(a) \quad -6i_1 + 8i_{sc} = +16 \rightarrow ②$$

Solving ① & ②

$$I_N = I_{sc} = 156/18$$

$$= 8.67 \text{ Amps}$$

to find R_N

With sources set to zero




$$R_N = 2 \text{ in series with } 12 \parallel 6$$

$$= 2 + 4$$

$$= 6 \Omega$$

Hence, Norton eq. is


(2)

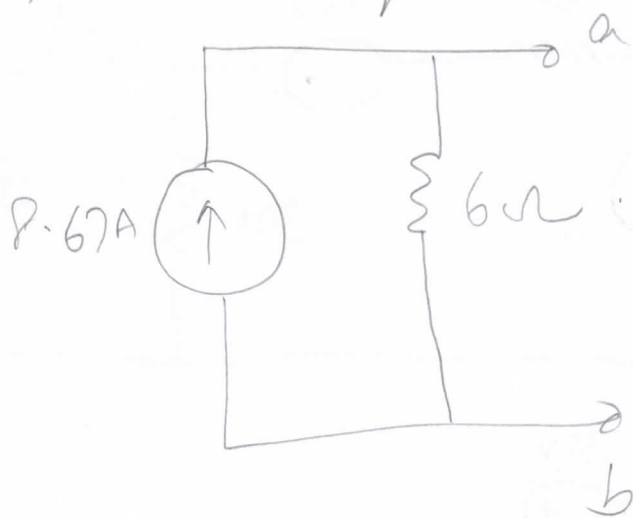


Pr
4.61

(3)

a)

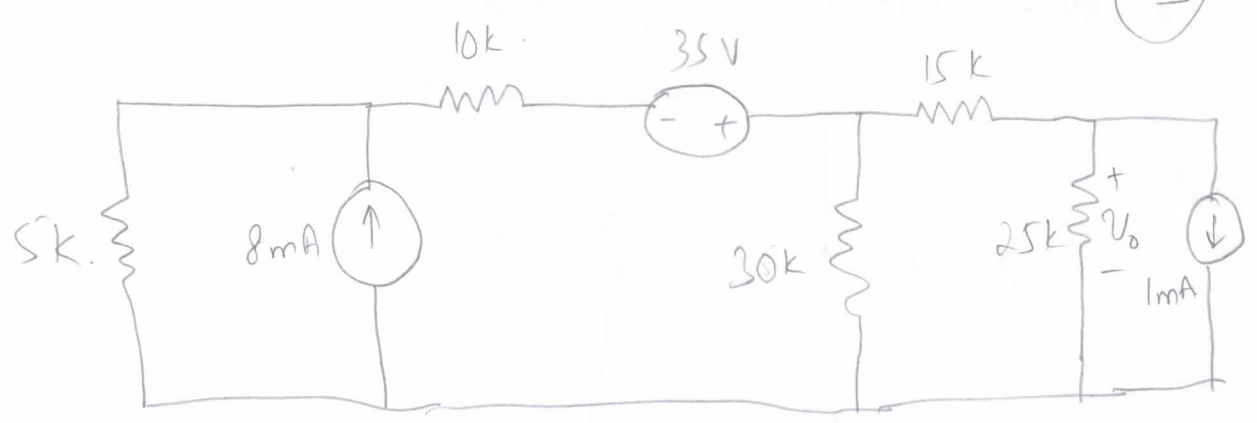


First
Step

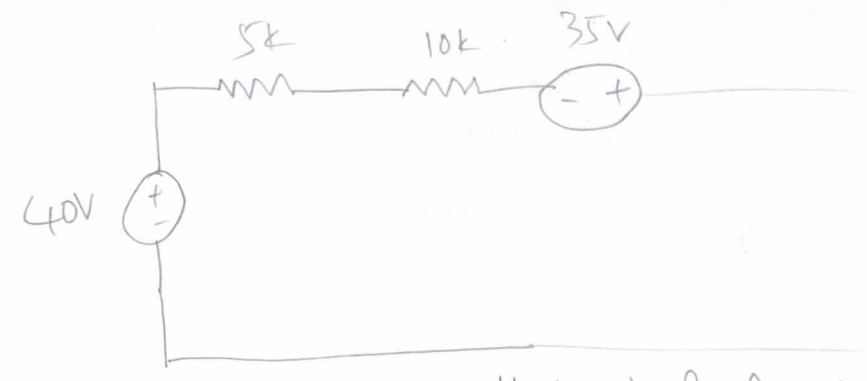


$5k$ in parallel with $8mA \Rightarrow 40V$ in series with $5k$.

Second
Step

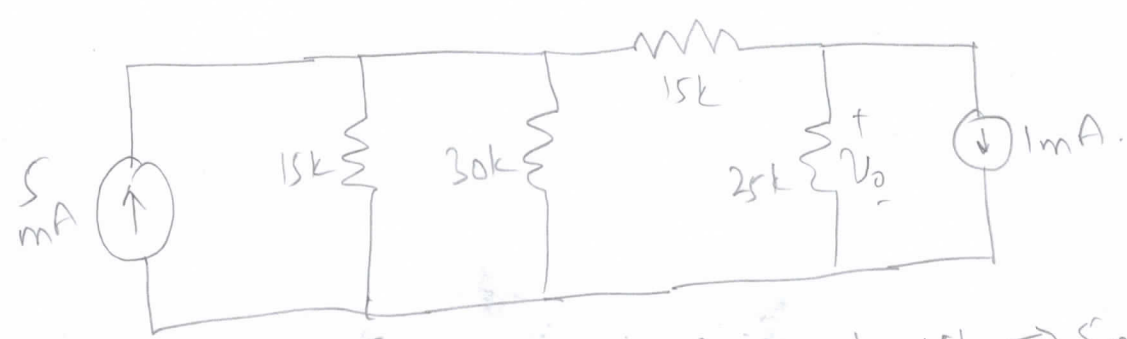


Add $40V + 35V$. $75V$ in series with $15k \Rightarrow 5mA$ in $\parallel 15k$.

Third
Step

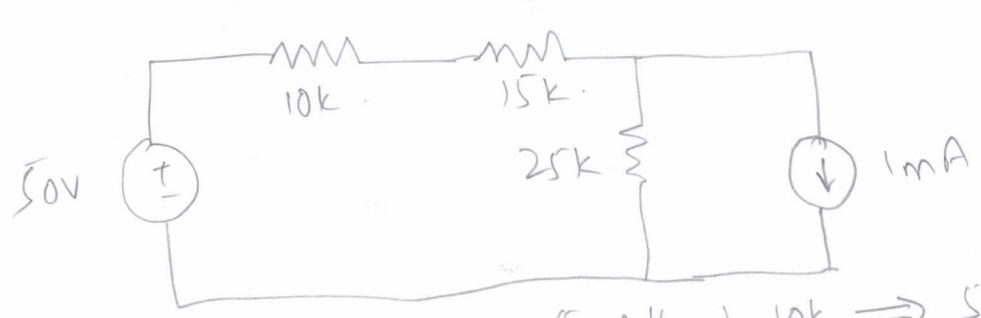


$15k \parallel 30k = 10k$. $5mA \parallel$ with $10k \Rightarrow 50V$ in series $10k$.

Fourth
Step

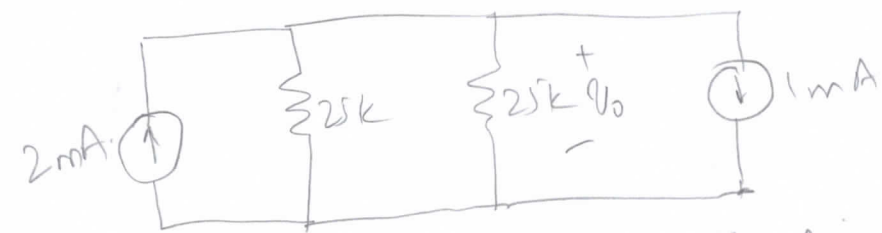


Final Step

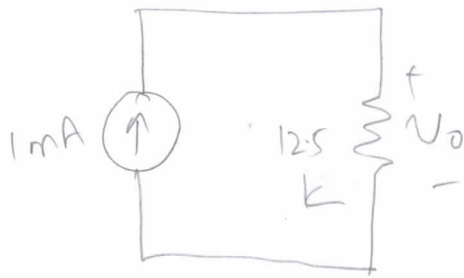

$$V_o = 12.5k \times 1mA$$

$$= 12.5 \text{ V}$$

b).

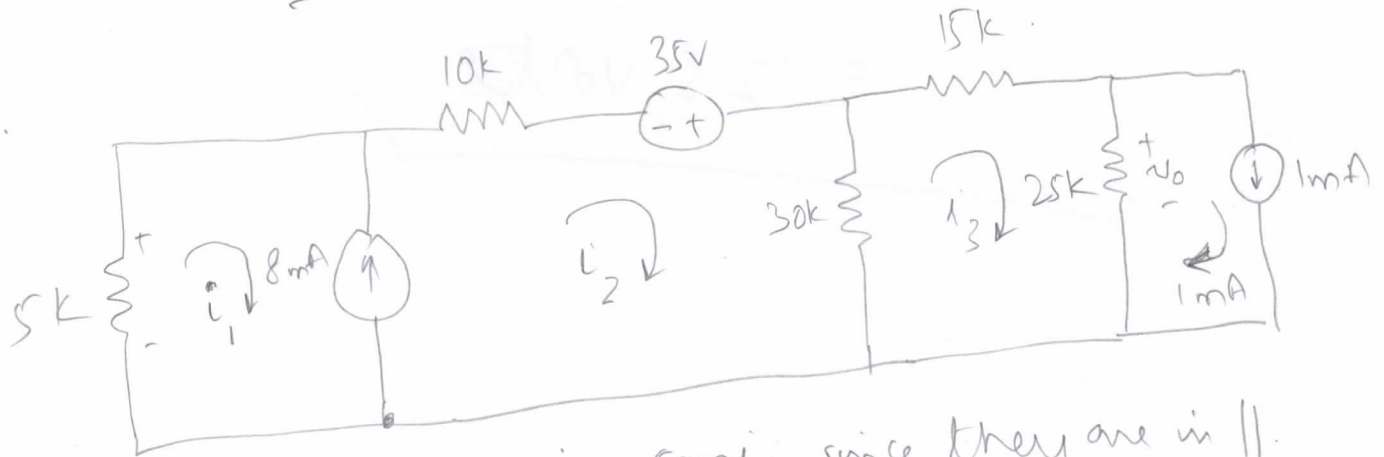

Voltage across 8mA source is $5000i_1$, since they are in ||.

Loop 1: $i_2 - i_1 = 8 \times 10^{-3} \rightarrow \textcircled{1}$

Loop 2: $5000i_1 + 10000i_2 - 35 + 30000(i_2 - i_3) = 0$

or $5000i_1 + 40000i_2 - 30000i_3 = 35 \rightarrow \textcircled{2}$

Loop 3: $-30000(i_2 - i_3) + 15000i_3 + 25000(i_3 - 1 \times 10^{-3}) = 0$

$-30000i_2 + 70000i_3 = 25 \rightarrow \textcircled{3}$

Put ① in ② $5000(i_2 - 8 \times 10^{-3}) + 40000i_2 - 30000i_3 = 35 \rightarrow \textcircled{2}$

or $45000i_2 - 30000i_3 = 75 \rightarrow \textcircled{2}$

$$i_3 = 1.5 \text{ mA}$$

$$i_2 = 2.667 \text{ mA}$$


$$i_1 = -5.33 \text{ mA}$$

$$\begin{aligned} \text{Hence: } V_o &= 25\text{k} * (i_3 - 1\text{mA}) \\ &= 25000 * (1.5 - 1) * 10^{-3} \\ &= 12.5 \text{ volts} \end{aligned}$$

Ch 4, Part B(2) Problems

[Page 1]

Pr 4.86

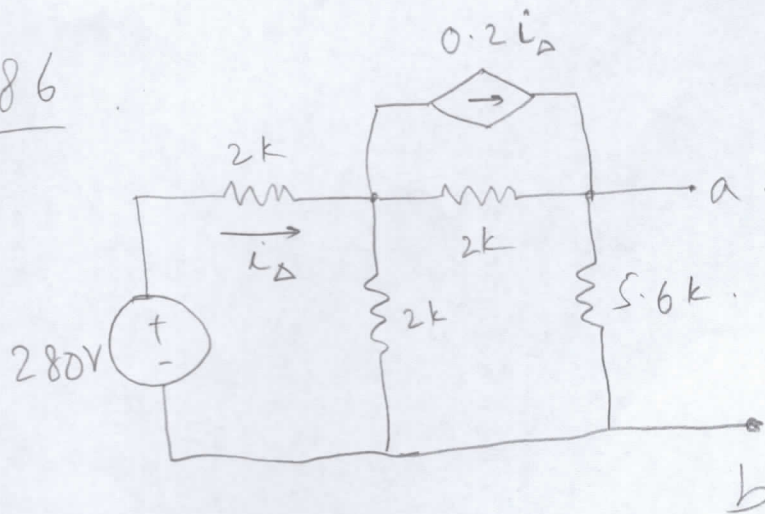


- a) find R_o for max power
- b) find max power
- c) % of total power to R_o .

② We must first create the Thevenin Equivalent of the above circuit.
i.e. we must find V_{th} & R_{in} . Then $R_o = R_{in}$.

first to find V_{th}

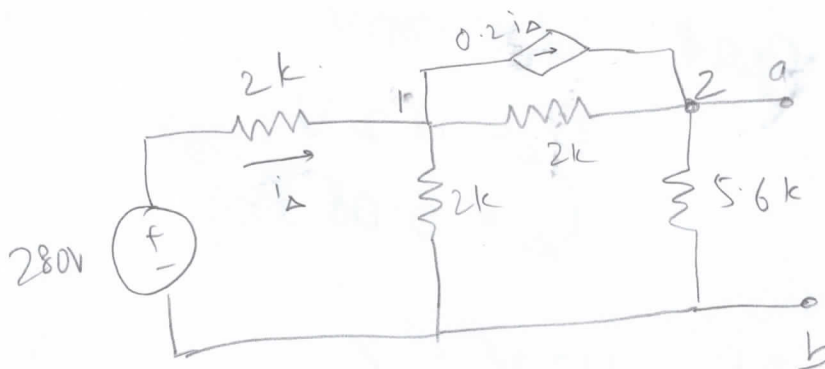Assume an open-circuit at terminals a and b, then find V_{ab} .



Name the two nodes 1 & 2.

KCL at Node 1

$$\frac{V_1 - 280}{2000} + \frac{V_1}{2000} + \frac{V_1 - V_2}{2000} + 0.2 i_{\Delta}' = 0$$

$$\frac{3V_1}{2000} - \frac{V_2}{2000} + 0.2 i_{\Delta}' = \frac{280}{2000} \quad \text{--- (1)}$$

KCL
at Node 2

$$\frac{V_2 - V_1}{2000} + \frac{V_2}{5600} - 0.2i_{\Delta} = 0$$

$$\text{or } -\frac{V_1}{2000} + \frac{19V_2}{28000} - 0.2i_{\Delta} = 0 \rightarrow (2)$$

Also :

$$-280V + 2k i_{\Delta} + V_1 = 0$$

$$\text{or } i_{\Delta} = \frac{280 - V_1}{2000} \rightarrow (3)$$

$$\frac{V_1}{2000} + i_{\Delta} = \frac{280}{2000} \rightarrow (3)$$

Solving (1), (2) & (3),

$$\text{we get } V_1 = 120V$$


$$V_2 = 112V$$

$$i_{\Delta} = 0.08A$$

$$V_{Th} = V_2 = 112V$$

Next, to find R_{Th}

$$R_{Th} = \frac{V_{Th}}{i_{sc}}$$

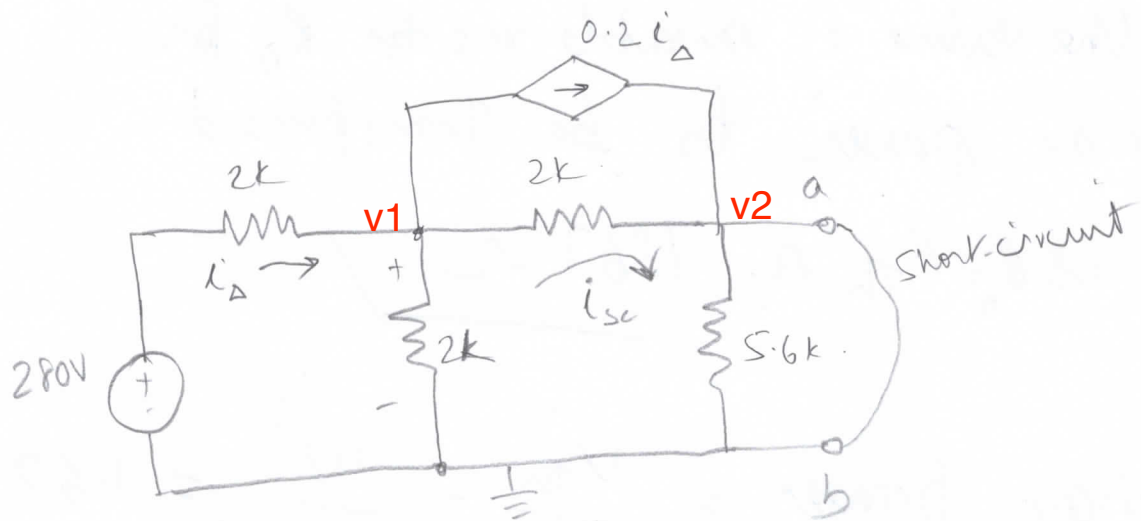

The two mesh-current equations are:

$$-280 + 2000i_{\Delta} + 2000(i_{\Delta} - i_{sc}) = 0$$

$$-2000(i_{\Delta} - i_{sc}) + 2000(i_{sc} - 0.2i_{\Delta}) = 0$$

$$4000i_{\Delta} - 2000i_{sc} = 280 \quad \rightarrow (1)$$


$$-2400i_{\Delta} + 4000i_{sc} = 0 \quad \rightarrow (2)$$

Solving: $i_{\Delta} = 0.1 \text{ A}$

$i_{sc} = 0.06 \text{ A}$

$$\text{So, } R_{th} = \frac{V_{th}}{i_{sc}} = \frac{112}{0.06} = 1866.67 \Omega$$

Thevenin
Equivalent
is

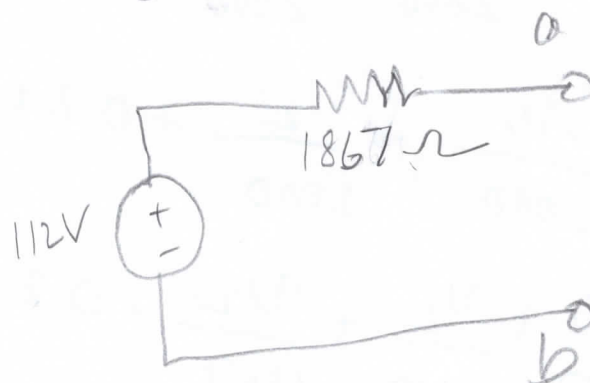


So, the value of variable resistor R_o for max power to be transferred

is $R_o = R_{Th} \approx 1867 \Omega$.

(b) Max power = $\frac{V_m^2}{4R_L} = \frac{112^2}{4 \times 1867} = 1.679 \text{ Watts}$

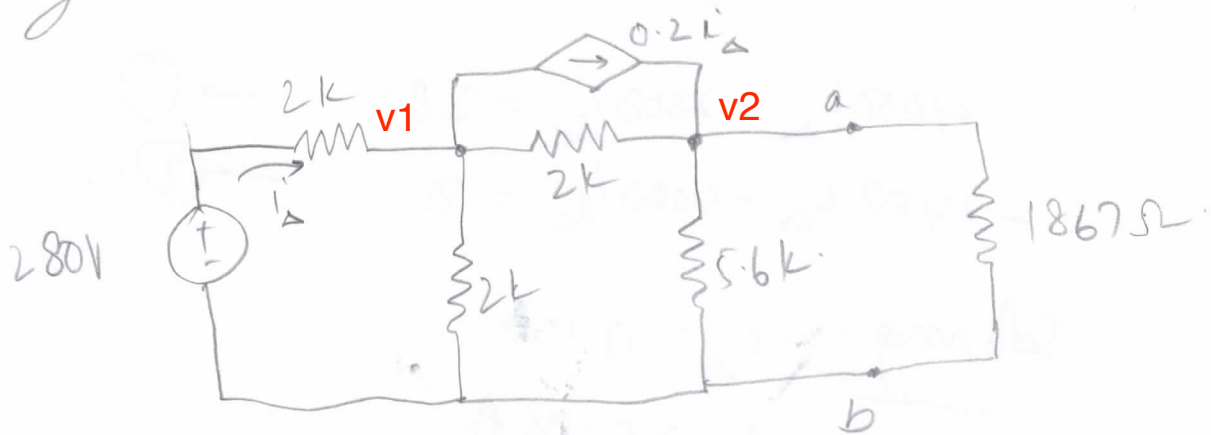(c) We have to first find total power generated in the circuit.



→ We have to find i_Δ , and voltage across Dep source.

KVL mesh 1: $\frac{v_1 - 280}{2000} + \frac{v_1}{2000} + \frac{v_1 - v_2}{2000} + 0.2i_\Delta = 0$

$\frac{3v_1}{2000} - \frac{v_2}{2000} + 0.2i_\Delta = \frac{280}{2000} \rightarrow \textcircled{1}$

KVL mesh 2: $\frac{v_2 - v_1}{2000} + \frac{v_2}{5600} + \frac{v_2}{1867} - 0.2i_\Delta = 0$

$$\text{or } -\frac{v_1}{2000} + \frac{24v_2}{28000} - 0.2i_{\Delta} = 0 \rightarrow \textcircled{2} \quad \textcircled{5}$$

$$\text{Also, } -280 + 2000i_{\Delta} + v_1 = 0 \quad \left(i_{\Delta} = \frac{280 - v_1}{2k} \right)$$

$$\text{or } \frac{v_1}{2000} + i_{\Delta} = \frac{280}{2000}$$

$$\text{or } v_1 + 2000i_{\Delta} = 280 \rightarrow \textcircled{3}$$

Solving ①, ② & ③ gives

$$v_1 = 100V, v_2 = 56V, i_{\Delta} = 90 \times 10^{-3} \text{ Amps.}$$

$$P_{280} = -(280)(0.09) = -25.2 \text{ W.}$$

$$P_{DS} = (v_1 - v_2) \times 0.2i_{\Delta} = 0.792 \text{ W.}$$

So, only P_{280} is providing power of 25.2 Watts.


Hence % of power going to R_0 is

$$\frac{1.68 \text{ W}}{25.2} \times 100 = \underline{\underline{6.67\%}}$$

Problem 4.92


Superposition

6

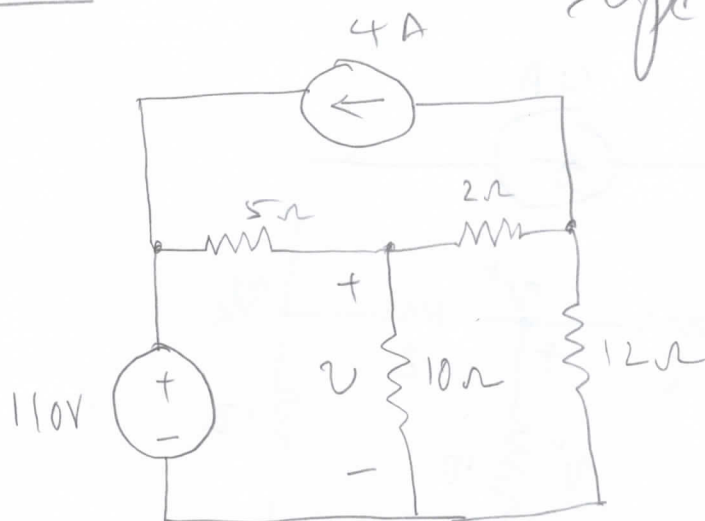

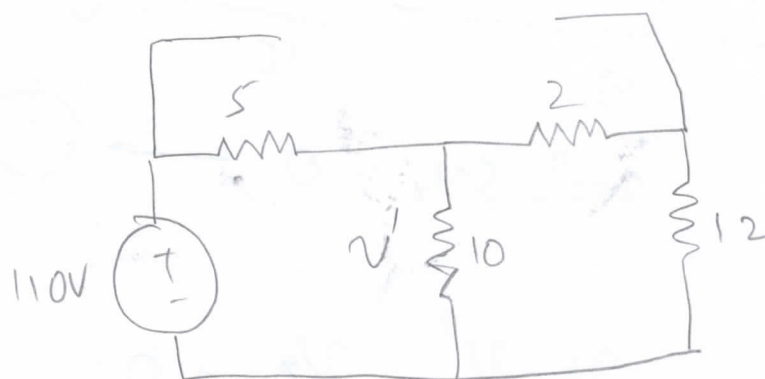a) find v . ($v = v' + v''$)

To use Superposition, we first disable the 4A source, and calculate v'




The 5Ω is in series with $10 \parallel (2+12)$, or
 5 in series with $35/6 \Omega$ (5.83Ω)

Using voltage divider formula:

$$v' = \left(\frac{5.83}{5 + 5.83} \right) \times 110 = 59.21 \text{ Volts}$$

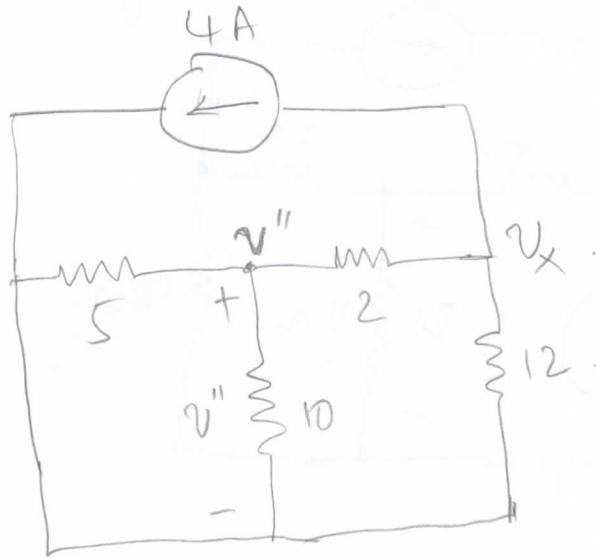Next, we disable 110V source and find v'' . (7)



Using Node-voltage method

KCL at v'' :

$$\frac{v''}{10} + \frac{v''}{5} + \frac{v'' - v_x}{2} = 0$$

$$\frac{v'' + 2v'' + 5v''}{10} - \frac{5v_x}{10} = 0$$

$$8v'' - 5v_x = 0 \rightarrow (1)$$

KCL at v_x :

$$4 + \frac{v_x - v''}{2} + \frac{v_x}{12} = 0$$

$$\frac{6v_x - 6v'' + v_x}{12} = -4$$

$$-6v'' + 7v_x = -48 \rightarrow (2)$$

Solving (1) & (2), gives $v'' = -9.2307$ Volts

8

$$\begin{aligned}\text{Hence: } V &= V' + V'' \\ &= 59.21 - 9.23 \\ &\approx 50 \text{ volts}\end{aligned}$$

$$\begin{aligned}\textcircled{b} \text{ Power in the } 10\Omega \text{ resistor} \\ &= \frac{V^2}{R} \\ &= \frac{50^2}{10} \\ &= 250 \text{ Watts}\end{aligned}$$
