

Quiz 3 - PrequizReview

Chapters 9 – 10

Chapters 9 - 10

9. Sinusoidal Steady State Analysis

10. Sinusoidal Steady-State Power Calculations

Chapter 9 – Sinusoidal Steady-State Analysis


Main ideas:

- The Sinusoidal Source

$$v = V_m \cos(\omega t + \phi)$$

$$f = \frac{1}{T}$$

$$\omega = 2\pi f$$

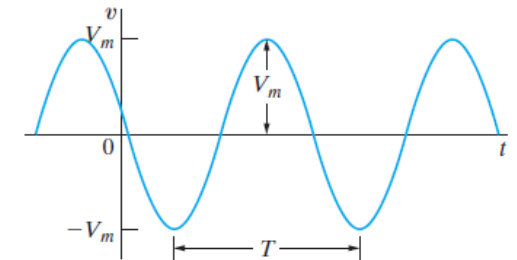


- Complex Numbers

$$z = x + jy \quad \text{Rectangular form}$$

$$z = r \angle \phi \quad \text{Polar form}$$
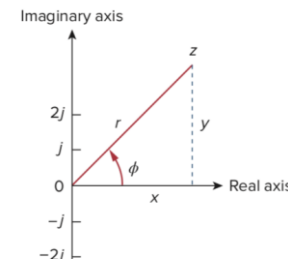
$$z = re^{j\phi} \quad \text{Exponential form}$$



Complex number arithmetic

- The Phasor

$$v(t) = V_m \cos(\omega t + \phi)$$

(Time-domain representation)

$$\mathbf{V} = V_m \angle \phi$$

x jy

- Passive Circuit Elements in the Frequency Domain

$$V = RI$$

$$V = j\omega LI$$

$$I = j\omega CV$$

Circuit Element	Impedance	Reactance
Resistor	R	—
Inductor	$j\omega L$	ωL
Capacitor	$j(-1/\omega C)$	$-1/\omega C$

- KVL & KCL, Series-Parallel Equivalent

$$\mathbf{Z}_{eq} = \frac{\mathbf{V}}{\mathbf{I}} = \mathbf{Z}_1 + \mathbf{Z}_2 + \dots + \mathbf{Z}_N$$

$$\frac{1}{\mathbf{Z}_{eq}} = \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} + \dots + \frac{1}{\mathbf{Z}_N}$$



$$\mathbf{V}_1 + \mathbf{V}_2 + \dots + \mathbf{V}_n = 0$$

$$\mathbf{I}_1 + \mathbf{I}_2 + \dots + \mathbf{I}_n = 0$$


Chapter 9 – Sinusoidal Steady-State Analysis

Main ideas:

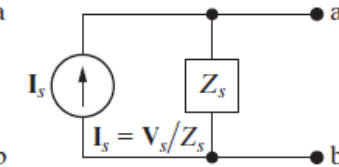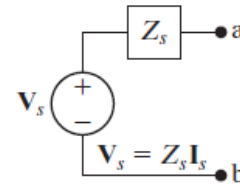
- Source Transformations, Thevenin & Norton Equivalents




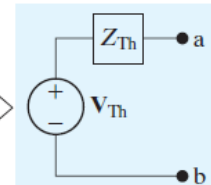
Frequency-domain linear circuit; may contain both independent and dependent sources.



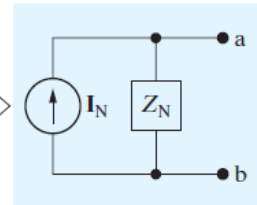
Frequency-domain linear circuit; may contain both independent and dependent sources.



- Node Voltage & Mesh Current Methods

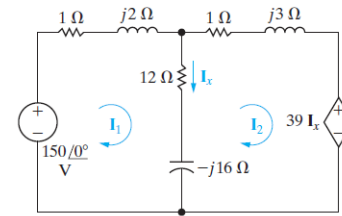
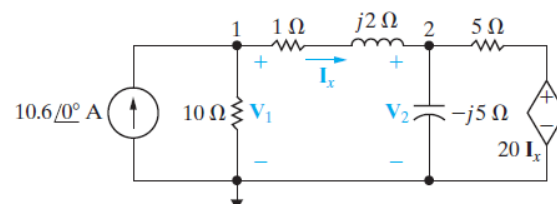


- Superposition

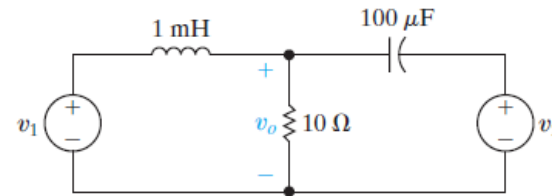

Sources with different ω


- The Transformer (Linear & Ideal)

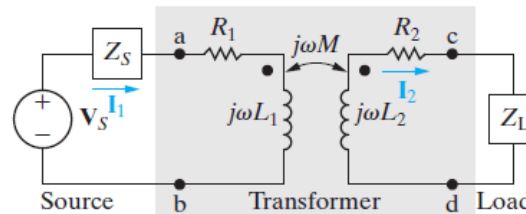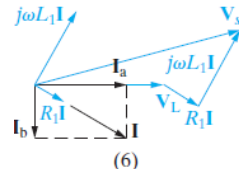

$$Z_{in} = \frac{V}{I_1} = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$

$$Z_{in} = R_1 + j\omega L_1 + Z_R$$
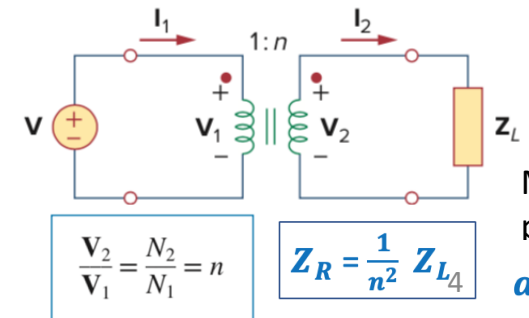
$$Z_R = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$




Max power
 $a^2 = \frac{Z_L}{Z_S}$

- Phasor Diagrams

Problem: Thevenin's Equivalent

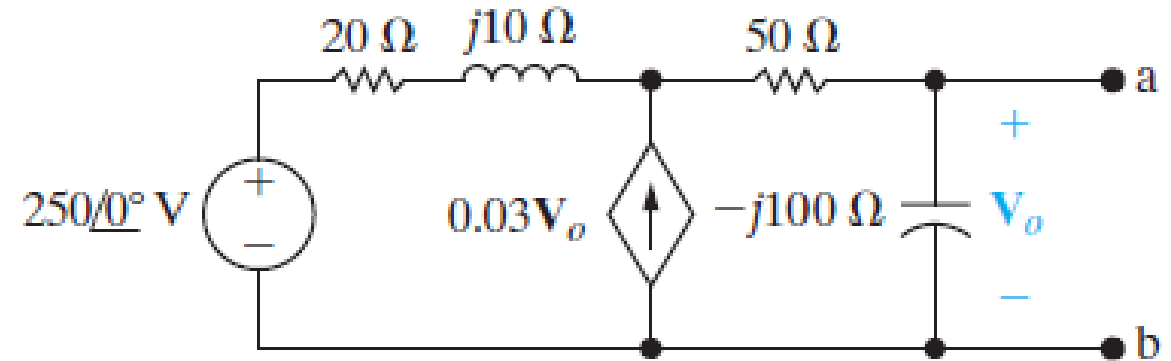Problem 9.50


Find the Thevenin equivalent circuit with respect to terminals a, b.



Problem: Node Voltage Method

Problem 9.57

Find V_o I_o


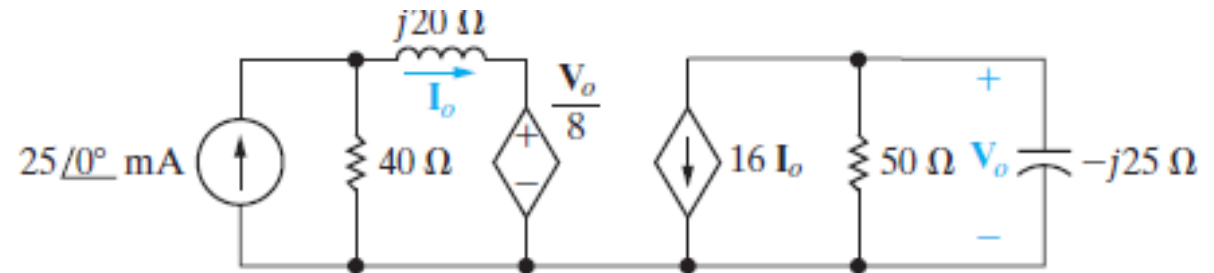


9.9 The Mesh Current Method

Example 9.14

Example 9.14:


Find V_1 V_2 V_3

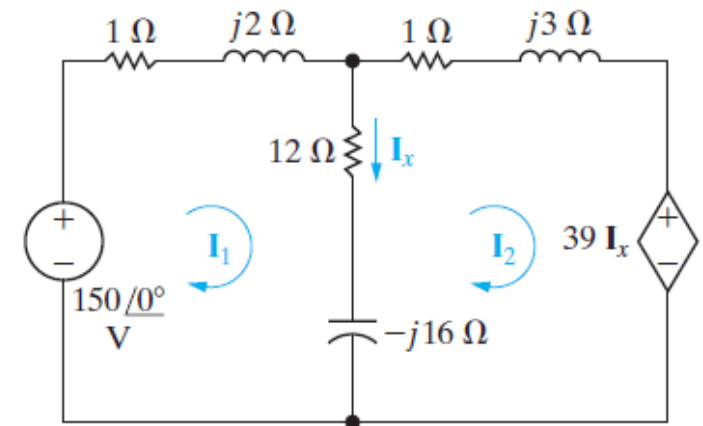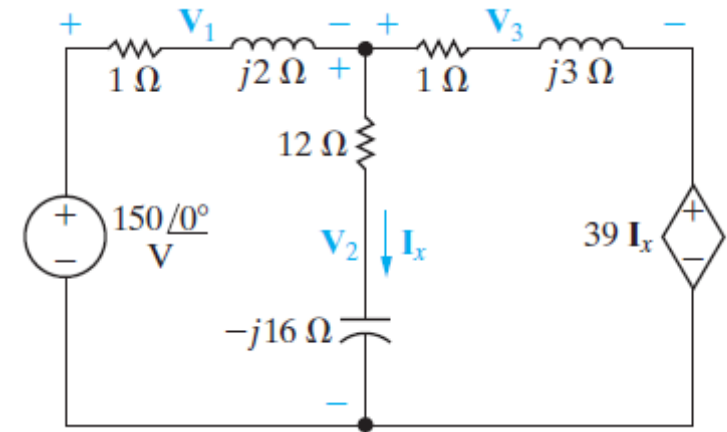

9.11 The Transformer, Ideal Transformer

Problem – Currents & Voltages

Find I_1 & V_o

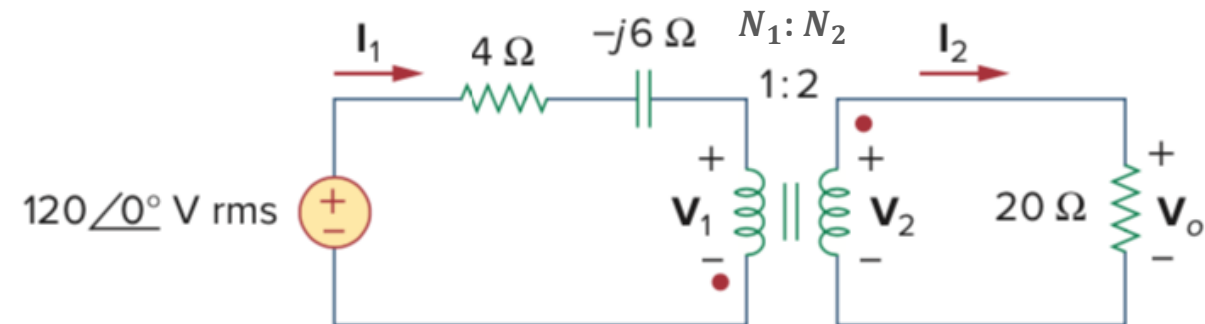

$$\frac{N_2}{N_1} = n$$

$$Z_R = \frac{1}{n^2} Z_L$$

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$

$$\frac{I_2}{I_1} = \frac{N_1}{N_2} = \frac{1}{n}$$

Chapter 10 – Sinusoidal Steady-State Power

Main ideas:

- Instantaneous Power

$$p(t) = \frac{1}{2}V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2}V_m I_m \cos(2\omega t + \theta_v - \theta_i)$$

- Average (or Real) and Reactive Power

$$P = \frac{1}{2}V_m I_m \cos(\theta_v - \theta_i) \longrightarrow \text{REAL POWER, in Watts}$$

+ve VARS for Inductance

$$Q = \frac{1}{2}V_m I_m \sin(\theta_v - \theta_i) \longrightarrow \text{REACTIVE POWER, in VARs}$$

-ve VARS for Capacitance

Also:

$$\theta = \theta_v - \theta_i$$

\longrightarrow POWER FACTOR ANGLE

$$\cos(\theta_v - \theta_i)$$

\longrightarrow POWER FACTOR

- Rms Value and Power Calculations

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

$$\text{(Real)} \quad P = \frac{1}{2}V_m I_m \cos(\theta_v - \theta_i) \quad \text{becomes} \quad P = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)$$


$$\text{(Reactive)} \quad Q = \frac{1}{2}V_m I_m \sin(\theta_v - \theta_i) \quad \text{becomes} \quad Q = V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)$$

- Complex Power



$$\begin{aligned} \text{Complex Power} = S &= P + jQ = \mathbf{V}_{\text{rms}}(\mathbf{I}_{\text{rms}})^* \\ &= |\mathbf{V}_{\text{rms}}| |\mathbf{I}_{\text{rms}}| \angle \theta_v - \theta_i \\ \text{Apparent Power} = S &= |\mathbf{S}| = |\mathbf{V}_{\text{rms}}| |\mathbf{I}_{\text{rms}}| = \sqrt{P^2 + Q^2} \\ \text{Real Power} = P &= \text{Re}(\mathbf{S}) = S \cos(\theta_v - \theta_i) \\ \text{Reactive Power} = Q &= \text{Im}(\mathbf{S}) = S \sin(\theta_v - \theta_i) \\ \text{Power Factor} = \frac{P}{S} &= \cos(\theta_v - \theta_i) \end{aligned}$$

Complex power \mathbf{s}

Q Reactive power

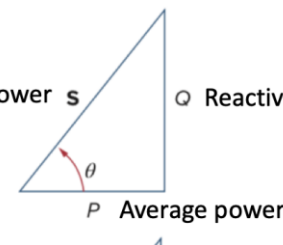

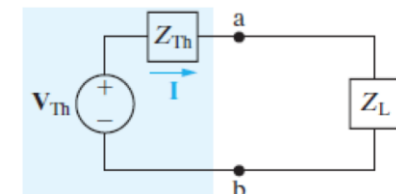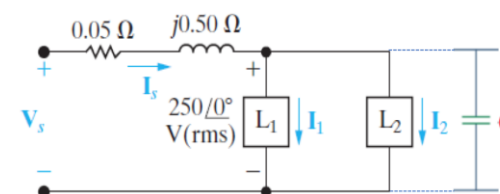- Power factor correction, Max Power Transfer




$$\mathbf{Z}_L = R_L + jX_L = R_{\text{Th}}^0 - jX_{\text{Th}} = \mathbf{Z}_{\text{Th}}^*$$

10.5 Power Calculations

Example 10.6 Calculating Average & Reactive Power

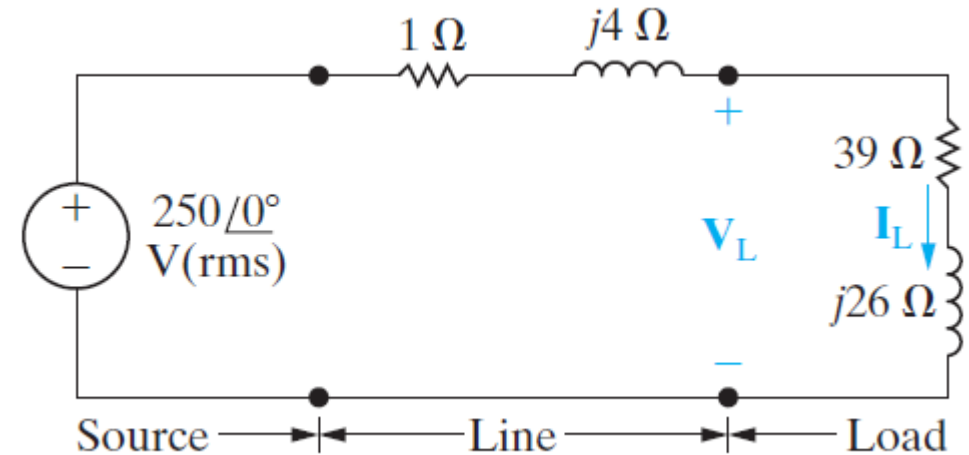- a) Calculate phasors V_L & I_L
- b) Calculate the reactive & average powers delivered to the **load**
- c) Calculate the reactive & average powers delivered to the **line**
- d) Calculate the reactive & average powers supplied by the **source**



$$\mathbf{S} = \mathbf{V}_{\text{rms}}(\mathbf{I}_{\text{rms}})^*$$

$$\mathbf{S} = P + jQ$$

$$\mathbf{S} = |\mathbf{I}_{\text{rms}}|^2 \mathbf{Z}$$

10.5 Power Calculations

HW problem 3

Problem 3:

When connected to a 120 V (rms), 60-Hz power line, a load absorbs 4kW at a lagging power factor of 0.8. Find the value of Capacitance, C, necessary to raise the power factor to 0.95 lagging.

$$\text{So } X_C = \frac{120^2}{1685.6} = 8.54 \Omega.$$

Maximum Power Transfer

Problem 10.44

- a) What is the maximum average power transferred to Z_L ?
- b) What percentage of the total power developed is transferred to the load impedance found above?

