

Lab Section (Day/Time) _____

Names of Student with ID# 2022214880

Student Li Xianzhe

Instructor signature _____

NAU + CQUPT

EE 188 Lab 8

Complex Power in AC Circuits

Introduction:

In **passive AC circuits** with both reactive and resistive elements (inductors, capacitors and resistors), **Power** must be **complex-valued** in order to account for the energy expended in actual work (Watts) and that which is tied-up in the maintenance of expanding and collapsing electric and magnetic fields in the reactive elements (Vars).

Complex Power in sinusoidal signals is best accounted for by using **complex-valued** notation.

The formula for **complex power S** in a circuit with a current and voltage at a port is given by

$$S = \frac{1}{2} VI^* \text{ (VA)}$$

where $V = V/\theta_v$ is the **voltage phasor** (V)

$I = I/\theta_i$ is the **current phasor** (A)

Phase angles θ_v and θ_i are with respect to a reference 0° elsewhere.

Note that the phasors are **peak values** and **not rms values** in this expression. If **rms values** are used, the $\frac{1}{2}$ factor would already be accounted for. For this exercise, we shall stick with **peak values**.

In **rectangular** and **polar** forms **S** is also expressed by

$$S = P + jQ$$

where **P = real power** (Watts)

Q = reactive power (Vars)

$$S = S/\theta_p$$

where **S = apparent power** (VA)

$\theta_p = \text{power angle} = (\theta_v - \theta_i)$ (electrical degrees)


The factor **$\cos(\theta_p)$** is defined as the **power factor (PF)**, and is an indication of the amount of available **real power** (of the **apparent power S**) that can be **delivered** or **absorbed** by the circuit at the input.

Procedure:

Set-up the following circuit, adjusting the function generator to

$$v_s(t) = 0.5 \cos(2\pi 500t) \text{ volts.}$$

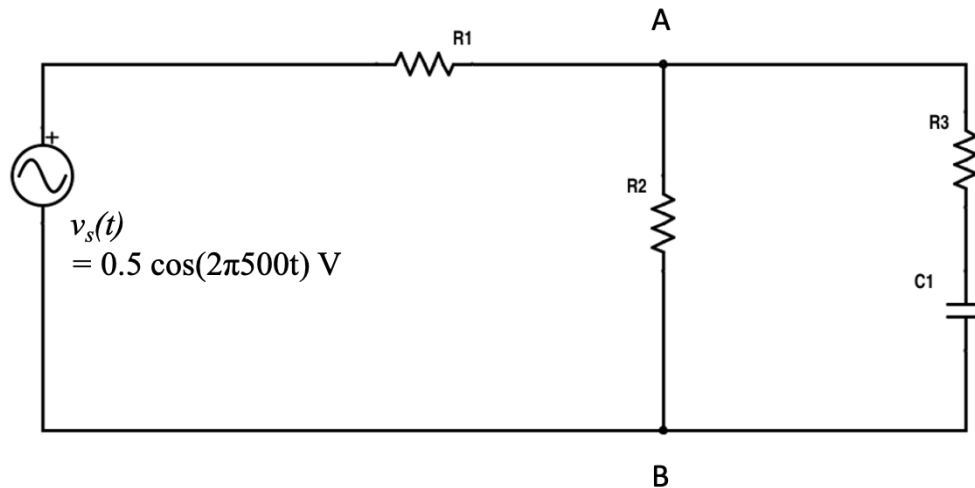Note that the **load** is between nodes **A** and **B**, which is **R₂** in parallel with the **R₃ - C₁** branch.



Measure and note the exact resistor and impedance values:

$$R_1 = 2.7\text{k}\Omega \Rightarrow \underline{2701.7\Omega} \text{ (measured)}$$

$$R_2 = 3.6\text{k}\Omega \Rightarrow \underline{3693.3\Omega} \text{ (measured)}$$

$$R_3 = 4.3\text{k}\Omega \Rightarrow \underline{4288.6\Omega} \text{ (measured)}$$

$$C_1 = 0.1\mu\text{F} \rightarrow Z_C = -j/\omega C = \underline{-j3183.1\Omega}$$

Activities A, B & C

A. Phasor, Impedance & Power Calculations:

- 1) Calculate Z_{Load} (show all steps, as done in lectures)
- 2) Calculate Z_T .
- 3) Calculate total current I_T .
- 4) Using **voltage division**, calculate V_{Load} .
- 5) Calculate total complex power S_T
- 6) Calculate load complex power S_{Load} .
- 7) Show that the **total complex power** equals the **load complex power** + the **real power** in resistor R_1 (which will also have to be calculated).

$$1). Z_L = (R_3 + Z_{C1}) \parallel R_2 = \frac{(4200 - j3183.1) \times 2700}{(4200 - j3183.1) + 2700} = 2188.6 - j568.7 \Omega$$

$$2). Z_T = Z_L + R_1 = 2188.6 - j568.7 + 2700 = 4888.6 - j568.7 \Omega$$

$$3). I_T = \frac{V_S}{Z_T} = \frac{0.5 \angle 0^\circ}{4888.6 - j568.7} = 1.02 \times 10^{-4} \angle 6.4^\circ \text{ A}$$

$$4). V_L = V_S \times \frac{Z_L}{Z_T} = 0.5 \angle 0^\circ \times \frac{2188.6 - j568.7}{4888.6 - j568.7} = 0.52 \angle -7.92^\circ \text{ V}$$

$$5). S_T = \frac{V_S \text{rms} I_T^*}{\sqrt{2}} = \frac{0.5^2}{\sqrt{2}} \angle (0^\circ - 6.4^\circ) = 0.52 \times 10^{-5} + j0.93 \times 10^{-6} \text{ VA}$$

$$6). S_L = \frac{V_L \text{rms} I_T^*}{\sqrt{2}} = \frac{0.52^2}{\sqrt{2}} \angle (-7.92^\circ - 6.4^\circ) = 1.13 \times 10^{-5} + j0.94 \times 10^{-6} \text{ VA}$$

$$7). P_{R1} = (I_T \text{rms})^2 R_1 = \left(\frac{1.02 \times 10^{-4}}{\sqrt{2}} \right)^2 \times 2700 = 1.4 \times 10^{-5} \text{ W}$$

$$S_L + P_{R1} = 0.52 \times 10^{-5} + j0.94 \times 10^{-6} \text{ VA} = S_T$$

B. Measurements:

Using both channels of your oscilloscope,

- 1) Measure the **input voltage signal** and use it as **reference 0°**
→ phasor $V_s = 0.5 \angle 0^\circ$ (volts)
- 2) Measure the **load voltage signal**:

$$V_L = 0.237 \angle -7.92^\circ \text{ V (phasor)}$$

and use it to calculate S_{Load} and S_T of **part A** above.

$$S_L = \frac{V_L I_L^*}{2} = \frac{(0.237 \angle -7.92^\circ) (1.2 \angle 5^\circ)}{2} = 1.2 \times 10^{-5} + j 3.12 \times 10^{-6} \text{ VA}$$

$$S_T = S_L + P_A = 1.2 \times 10^{-5} + j 3.12 \times 10^{-6} + 1.4 \times 10^{-5} = 2.6 \times 10^{-5} + j 3.12 \times 10^{-6} \text{ VA}$$

→ Clearly show all your steps and calculations, as done in class!

C. Drawing graphs:


Plot on the Complex (Re, Im) plane the 3 separate graphs below:

- 1) All **Impedance Vectors**, showing that they **add vectorally**

$$Z_T = Z_T \angle \phi_T = Z_{\text{Load}} + R_1$$

→ All units are in Ohms (Ω)

Example – drawing impedances

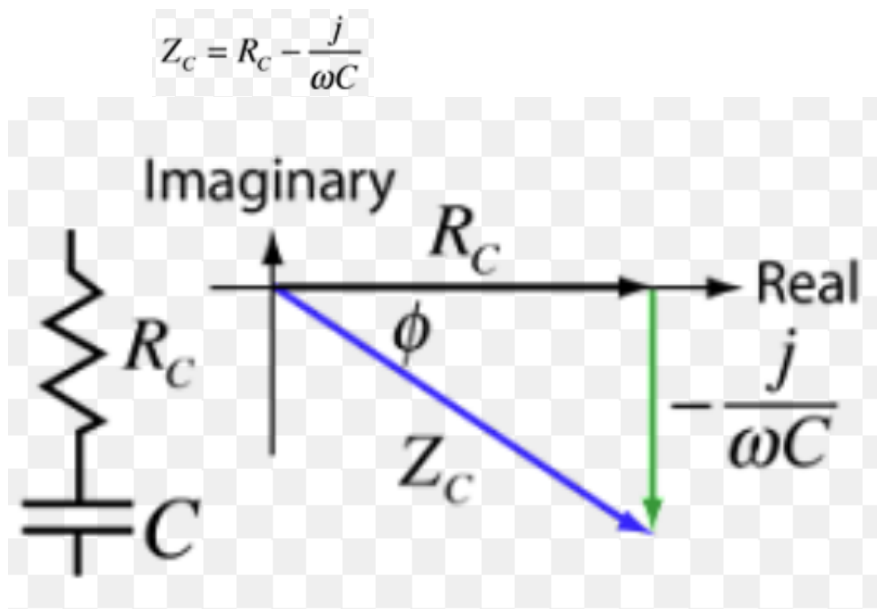


- 2) The **Complex Power Vectors**, showing that they **add vectorally**

$$S_T = S_L + P_{RI} = P_T + jQ_T$$


→ All units are Power units (VA, Vars & Watts)

Example – the power vector

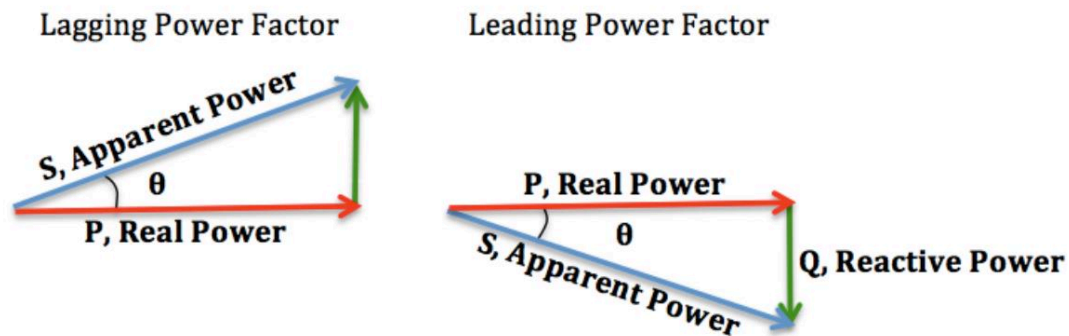


- 3) The **Phasor Vectors** for $V_s = 0.5/\underline{0^\circ}$ (ref), I_T and V_L .


Example – drawing phasors

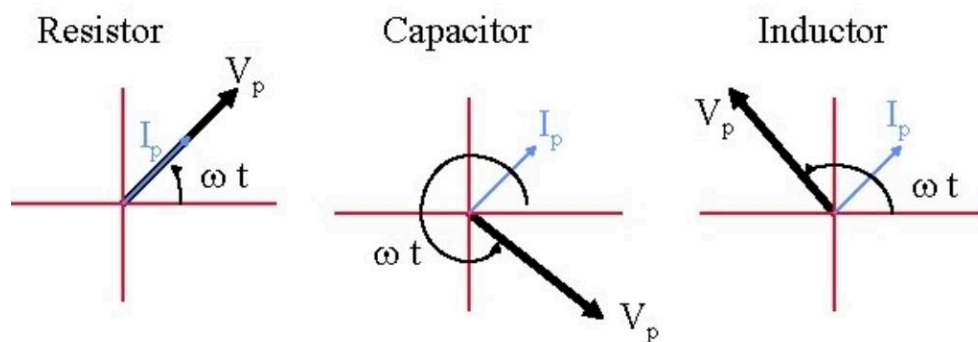

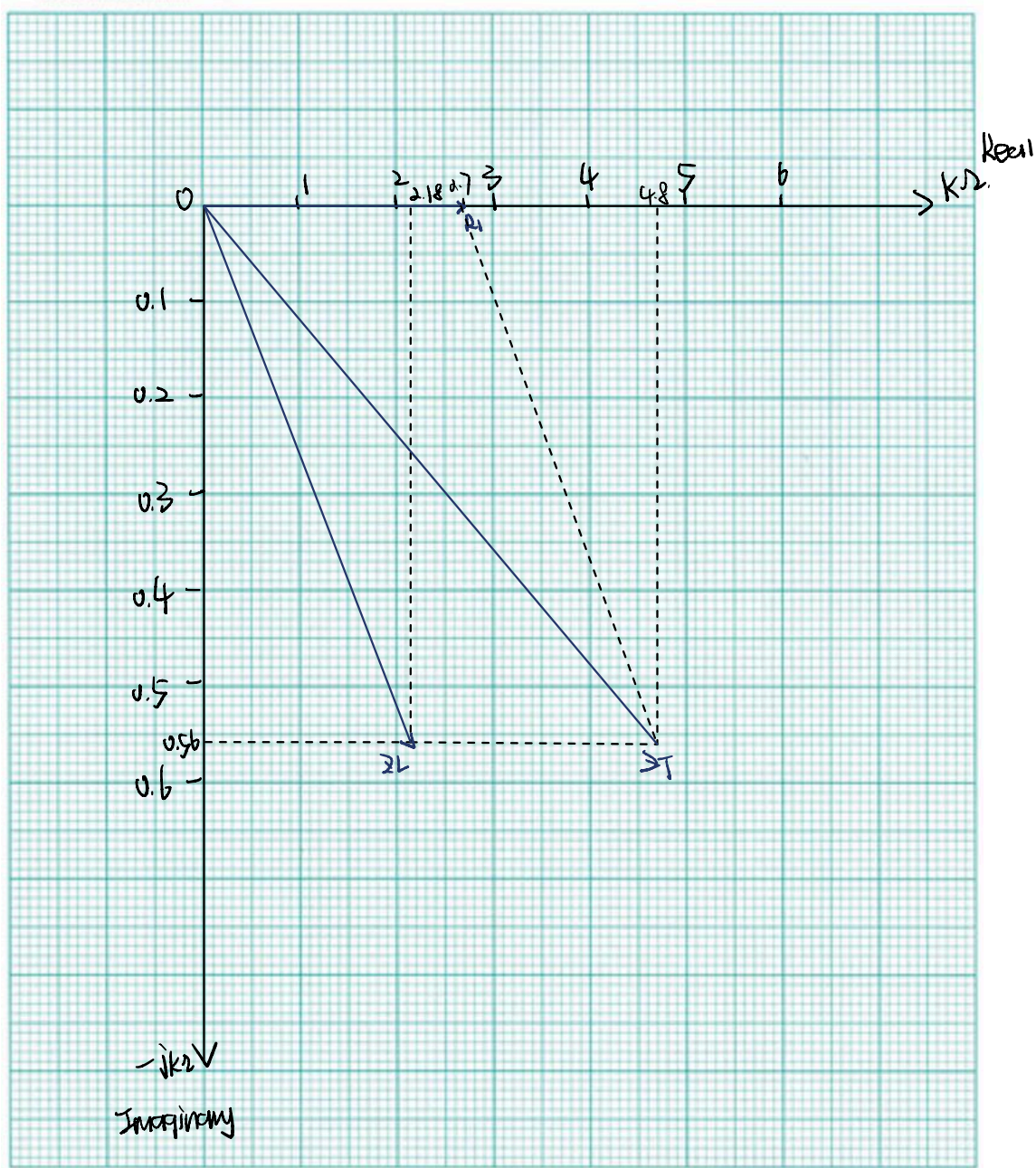
Note: You will have to put in the proper scales and units for x- and y-axis in each of the complex-plane graphs below



Impedance ($k\Omega$)

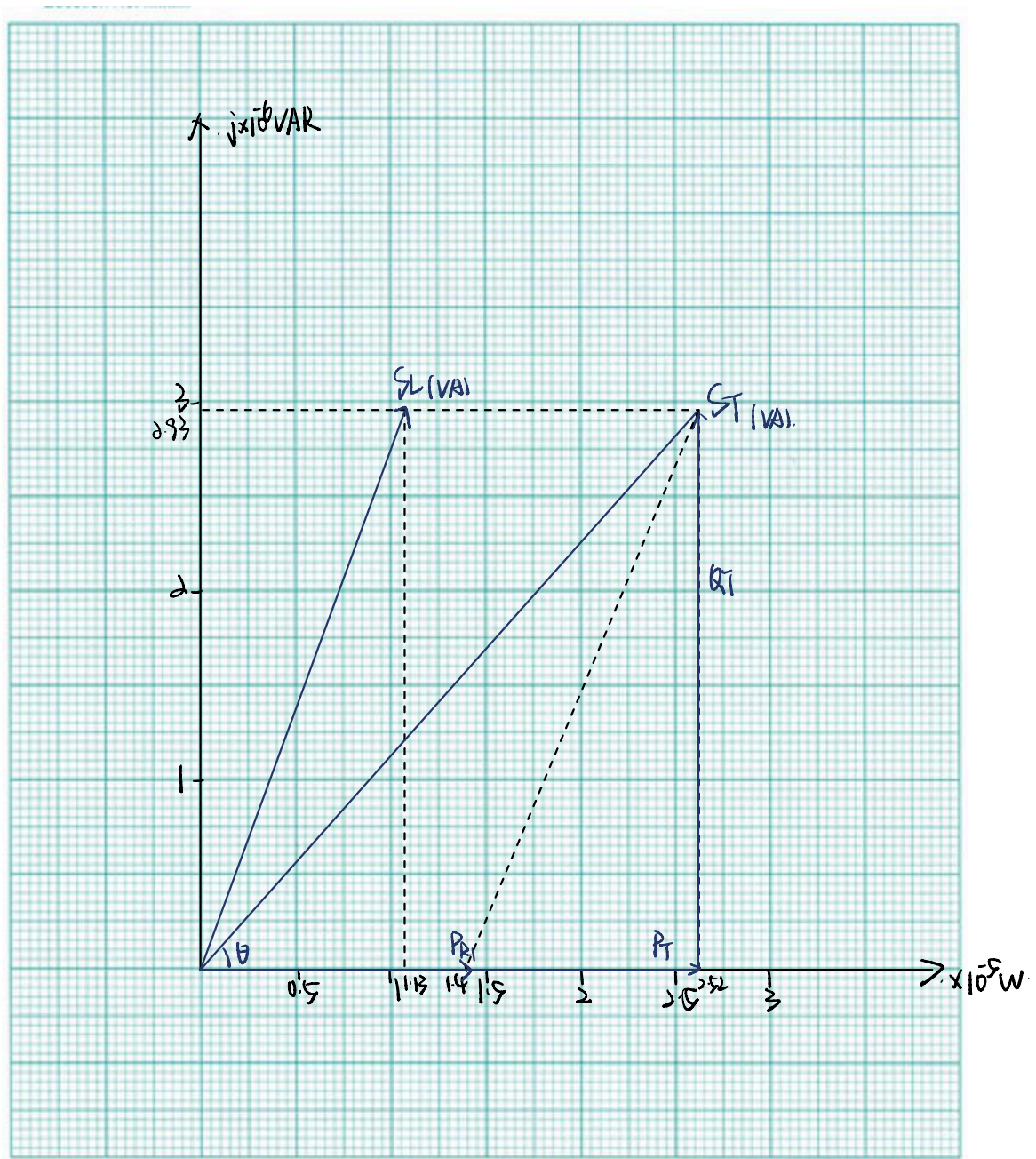

Complex Power (VA, Watts, Vars)

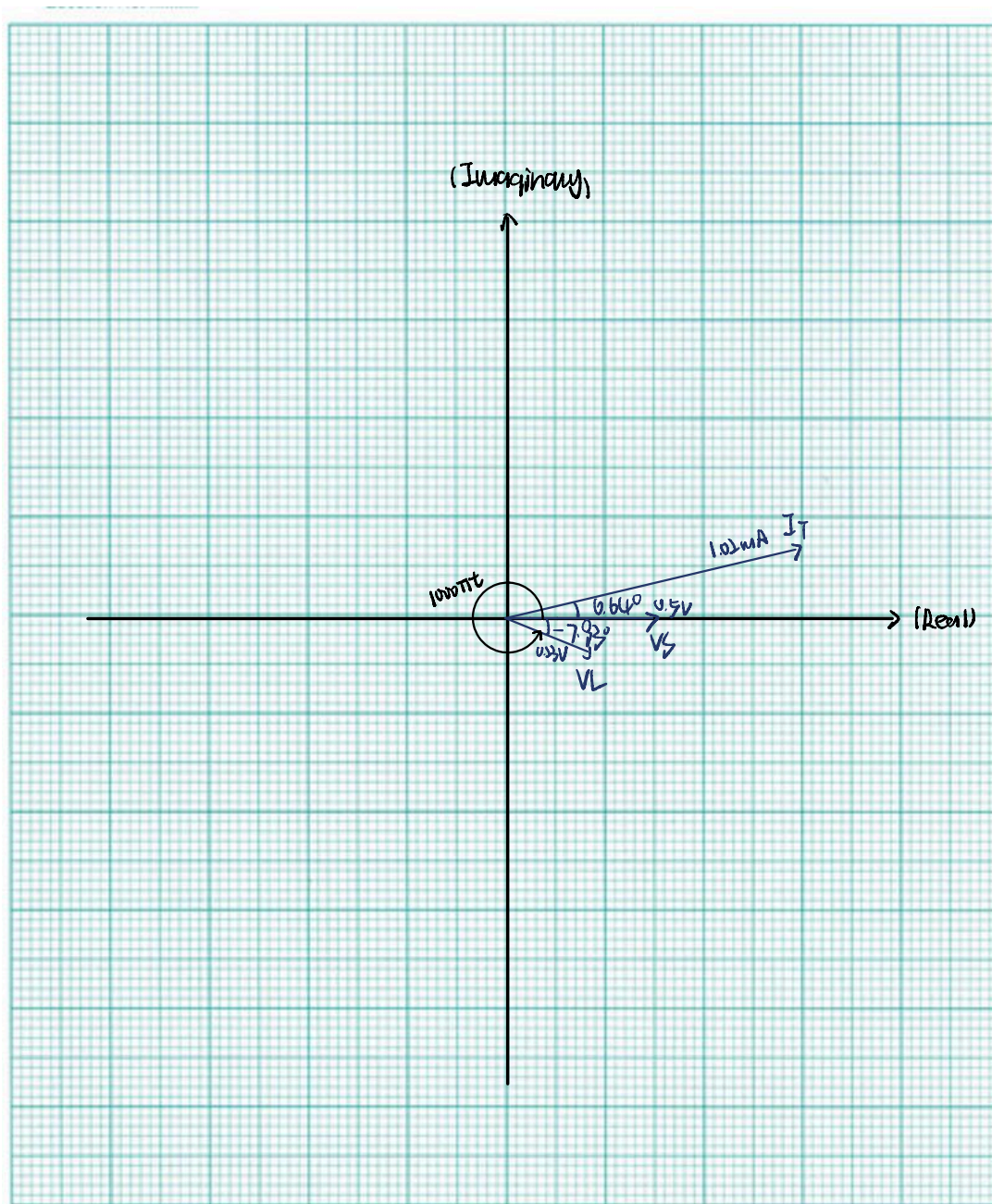

Phasors (volts & mA)

Lab Section (Day/Time) _____

Names of Student with ID# 202214880

Student Li Xianzhe

Instructor signature _____

NAU + CQUP

EE 188 Lab 8

Complex Power in AC Circuits

12/11